




FPGA系統設計

Control Unit



Modern Design (1/3)

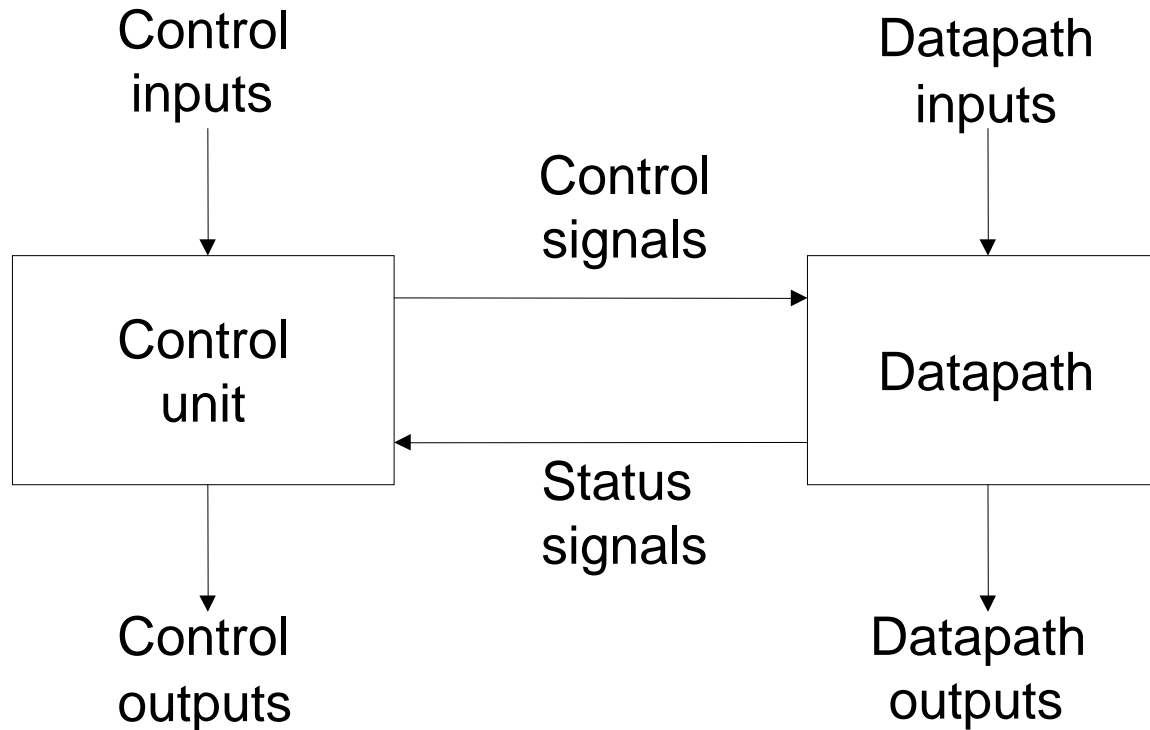Modern design is composed of (1) Datapath and
(2) Controller (control unit or control path)




(Note)

High-level block diagram




Modern Design (2/3)

Register-transfer-level block diagram

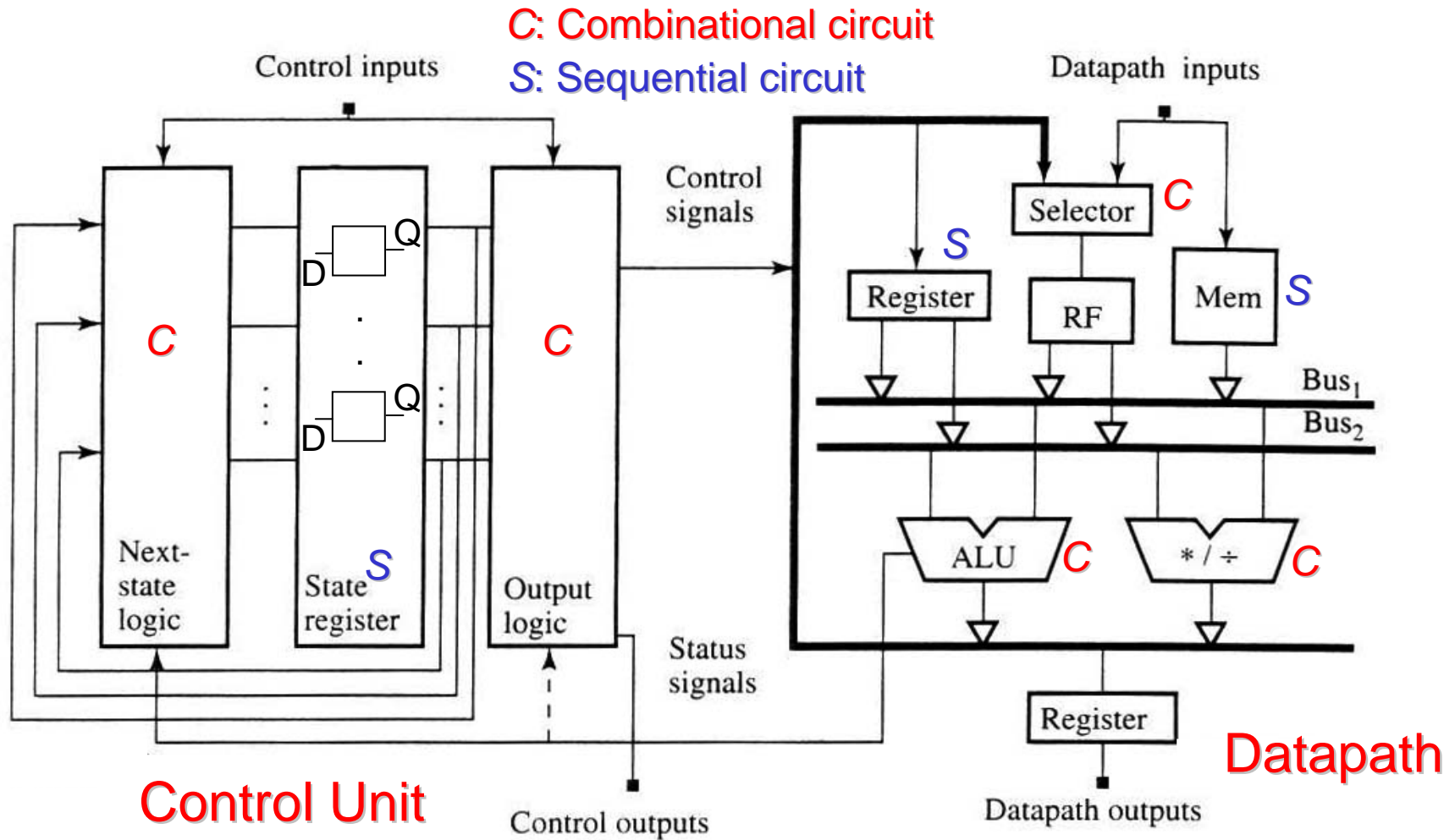

Modern Design (3/3)
 
```
if IR(3) = '0' then
    PC      := PC + 1;
else
    DBUF    := MEM(PC);
    MEM(SP) := PC + 1;
    SP      := SP - 1;
    PC      := DBUF;
end if;
```



An synthesis example of case statement

(a) HDL description

(b) Control-flow representation

(c) Data-flow representation

Case C is

When 1=> X := X+2;



A := X+5;

When 2=> A := X+3;

When others => A := X+W;

end case;


(a)

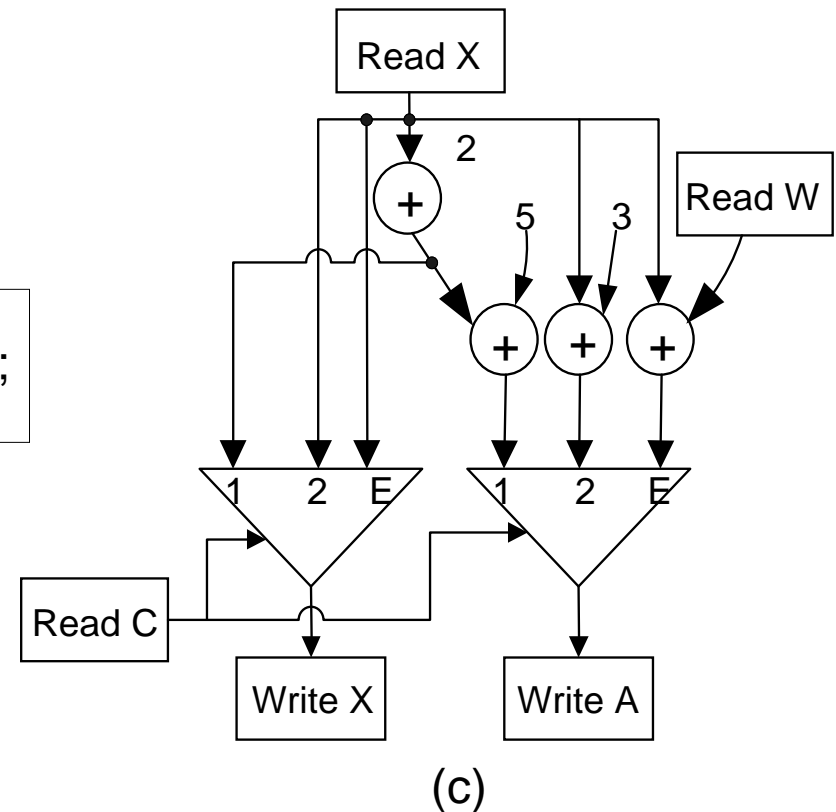 

Summation Problem (1/4)

Calculate $S = x_1 + x_2 + x_3 + x_4 + x_5$ with a ASIC chip

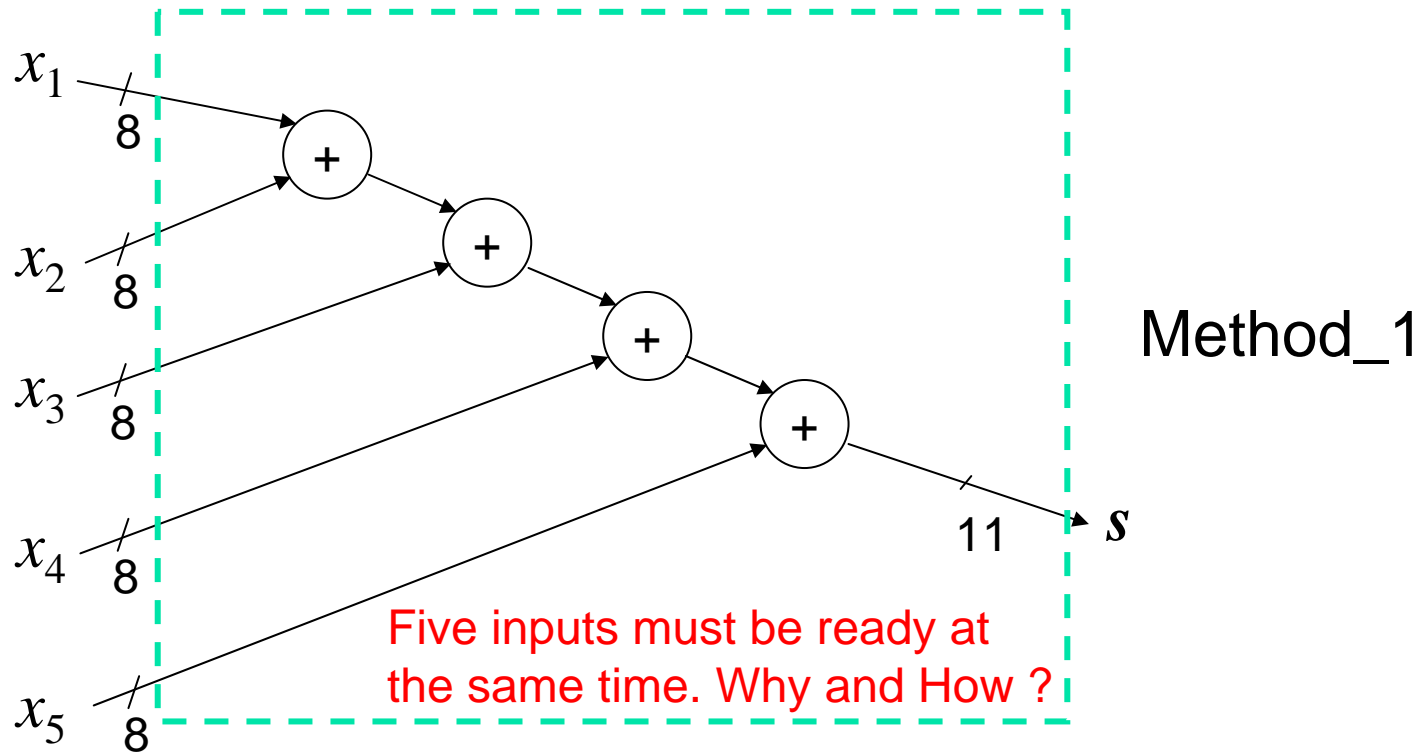1. Sum up five inputs in the same period by using 4 adders



- a. How many input pins and output pins ?
- b. What is the resolutions of x_i ?
- c. How fast you need ?
- d. What is your design cost ?

Summation Problem (2/4)

Calculate $S = x_1 + x_2 + x_3 + x_4 + x_5$

2. Sum up five inputs in the different time units by using only 1 adders

Initial $S = 0$


Time unit _1 $S \leq S + x_1$

Time unit _2 $S \leq S + x_2$

Time unit _3 $S \leq S + x_3$

Time unit _4 $S \leq S + x_4$

Time unit _5 $S \leq S + x_5$

 

Only one input must be ready at a time. Why?

Cost is lower and critical path is shorter than the Method_1 .


But its working rate is slower than Method_1. (5 clock cycles for 1 summation result)

Summation Problem (3/4)

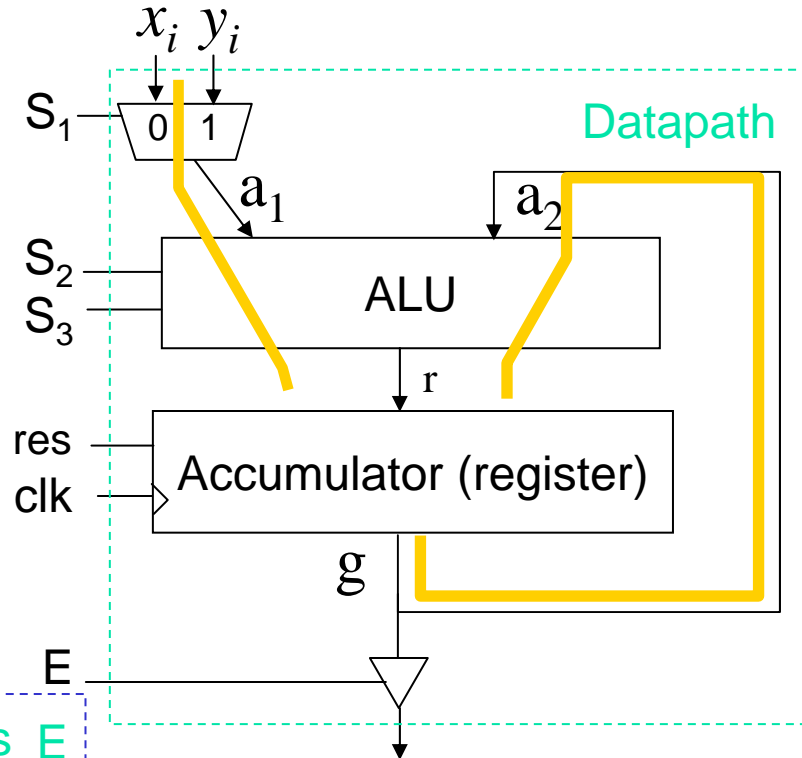Problem: Calculate $S = x_1 + x_2 + x_3 + x_4 + \dots + x_{50}$

$$S = \sum_{i=1}^{50} x_i$$


Control Unit
(send out proper control signals)



- If $S_1=0$, $a_1=x_i$
- If $S_1=1$, $a_1=y_i$
- If $S_2=0$ $S_3=0$, $r = a_2$
- If $S_2=0$ $S_3=1$, $r = a_1+a_2$
- If $S_2=1$ $S_3=0$, $r = a_1-a_2$
- If $S_2=1$ $S_3=1$, $r = a_1$

	S_1	S_2	S_3	res	E
T_0	0	0	0	1	0
T_1	0	1	1	0	0
T_2-49	0	0	1	0	0
.....					
T_51	X	0	0	0	1

New x_i must come now (e.g., x_2)

 

r must be ready before the next positive edge comes

What is the length of clock period (———)?
Critical (longest) path delay
⇒ 倒數為clock rate

Summation Problem (4/4)

Control unit should send out proper control signals at each state.

There are two ways to generate those control signals:

(1) Microprogramming control

a. Store control signals of each state at memory (ROM)

b. Read out the control signals one by one

(2) Hardwired control


Use dedicate logic gates to generate the proper signals state by state (one by one)

word →

	S ₁	S ₂	S ₃	res	E
T ₀	0	0	0	1	0
T ₁	0	1	1	0	0
T _{2~49}	0	0	1	0	0
.....					
T ₅₁	X	0	0	0	1

Clock Period (1/4)

Gate:	not	and	or	xor
Delay:	1ns	2.4ns	2.4 ns	4.2ns

 

R1(Registers,p-trigger)

R2(p-trigger)

longest path for stage 2

R3(p-trigger)

16.6 ns > 11.4ns


critical path=16.6 ns, so the clock period must be more than 16.6 ns (e.g., 18ns), why ?

New value for R1 is ready here
New value for R2 is ready here

Correct result for stage 1 must be ready here before next p-edge
Correct result for stage 2 must be ready here before next p-edge

need 11.4 ns


need 16.6 ns

 

New value for R2 is ready here
New value for R3 is ready here


Clock Period (2/4)

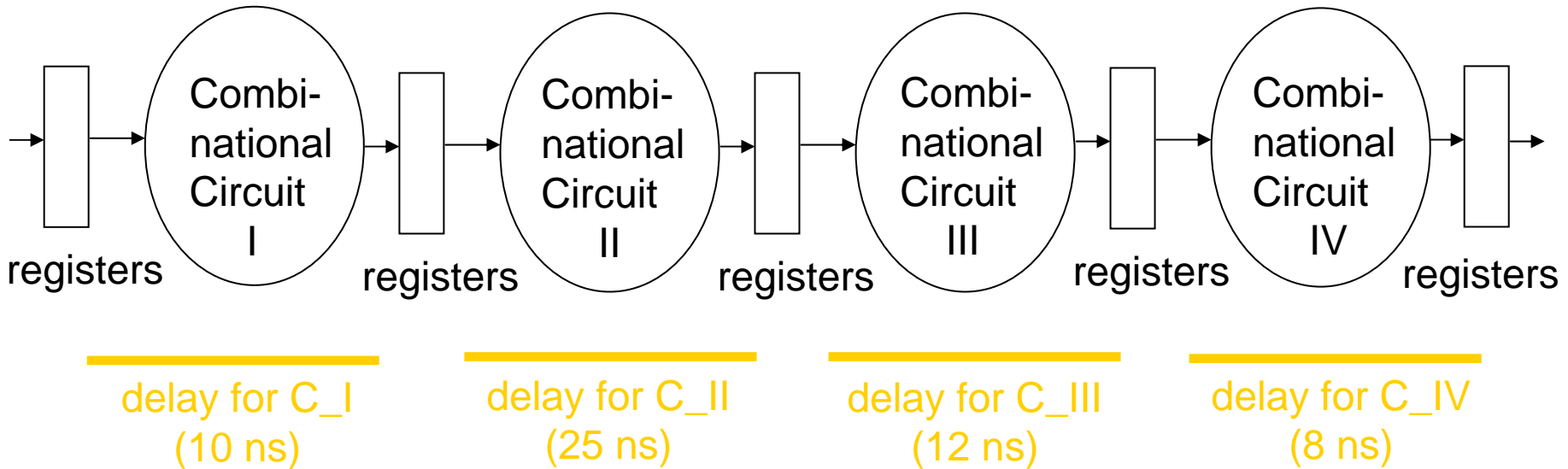How to decide the clock period in a system?



1. Find out the **longest delay** among combinational circuits C_I, C_II, C_III and C_IV.
2. The longest delay is named as the critical path (here is **25 ns**).
3. The clock period can be set as little longer than the critical path, why?
4. clock frequency = $\frac{1}{\text{clock period}}$ (here $\frac{1}{25\text{ns}} = \frac{1}{25 \times 10^{-9}} = 40 \text{ MHz}$)

Clock Period (3/4)

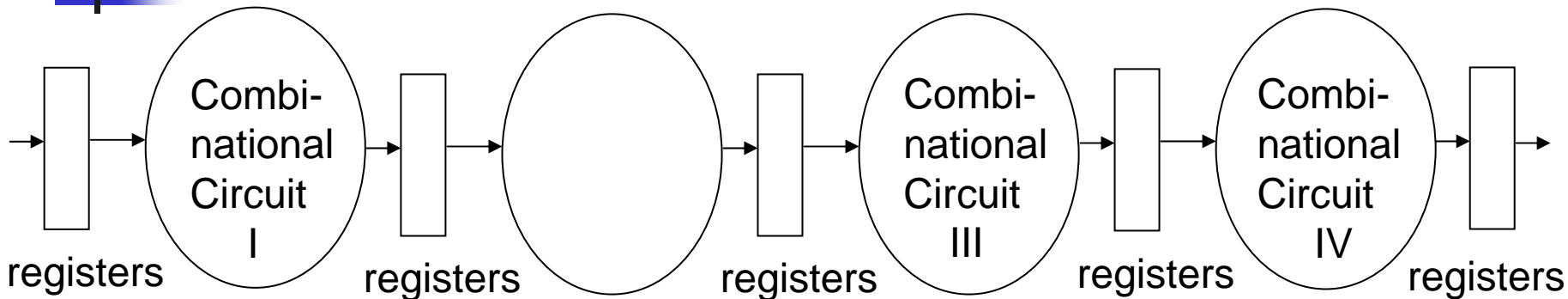


delay for C_I
(10 ns)

delay for C_II
(25 ns)

delay for C_III
(12 ns)

delay for C_IV
(8 ns)

Combinational
Circuit II

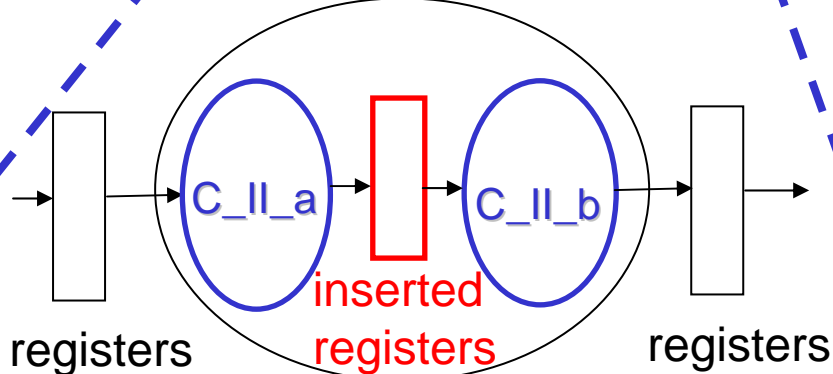

delay for C_II_a
(14 ns)


delay for C_II_b
(14 ns)

Separate C_II into two parts
(C_II_a and C_II_b) by
inserting proper registers to
achieve faster clock frequency

Now, clock frequency is 71.4 MHz

Clock Period (4/4)

 Better HDL style → Separating combinational and sequential circuits



```
module EXAMPLE(data1,data2,clk,q);  
input  data1, data2, clk;  
output q;  
reg    data,q;  
  
always @(data1 or data2)  
    data = com(data1,data2);  
  
always @(posedge clk)  
    q <= data;  
endmodule
```

Combinational
Logic

Sequential
Logic

Design for Summation Problem (1/7)

Method_1



```
module adder1(x1, x2, x3, x4, x5, out);  
input x1, x2, x3, x4, x5;  
output [2:0] out;  
reg [2:0] out;
```

```
always@(x1 or x2 or x3 or x4 or x5)
```

```
out=(((x1+x2)+x3)+x4)+x5;
```

```
endmodule
```

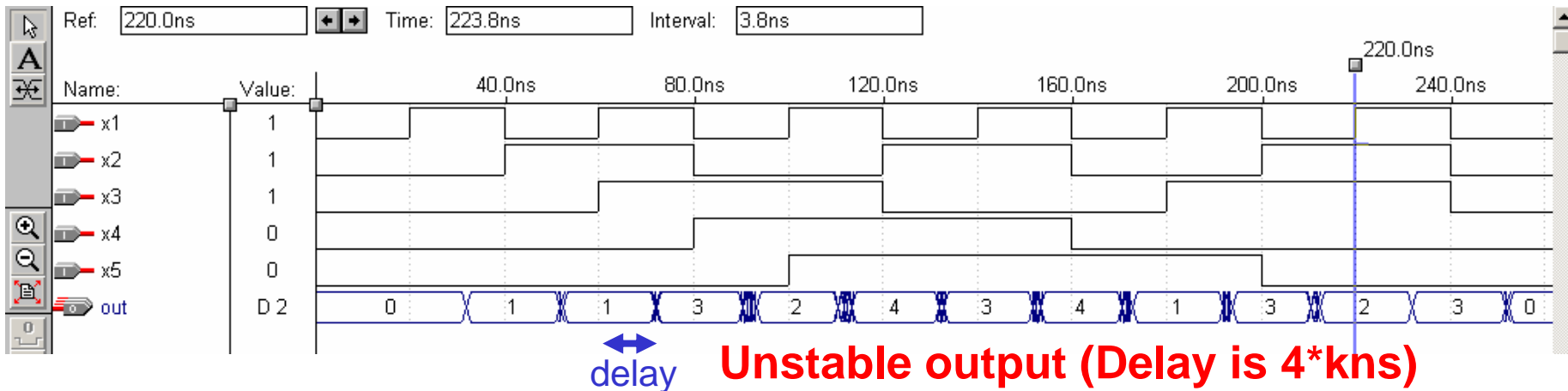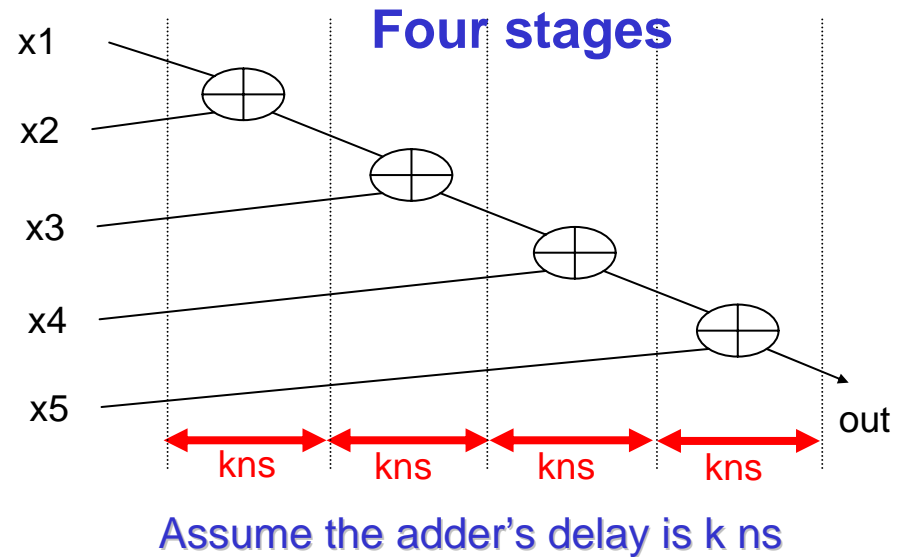Calculate $S = x_1 + x_2 + x_3 + x_4 + x_5$



Design for Summation Problem (2/7)

Method_2 (shorter delay)



```
module adder2(x1, x2, x3, x4, x5, out);  
input x1, x2, x3, x4, x5;  
output [2:0] out;  
reg [2:0] out;
```

```
always@(x1 or x2 or x3 or x4 or x5)
```

```
out=((x1+x2)+(x3+x4))+x5;
```

```
endmodule
```

Three stages

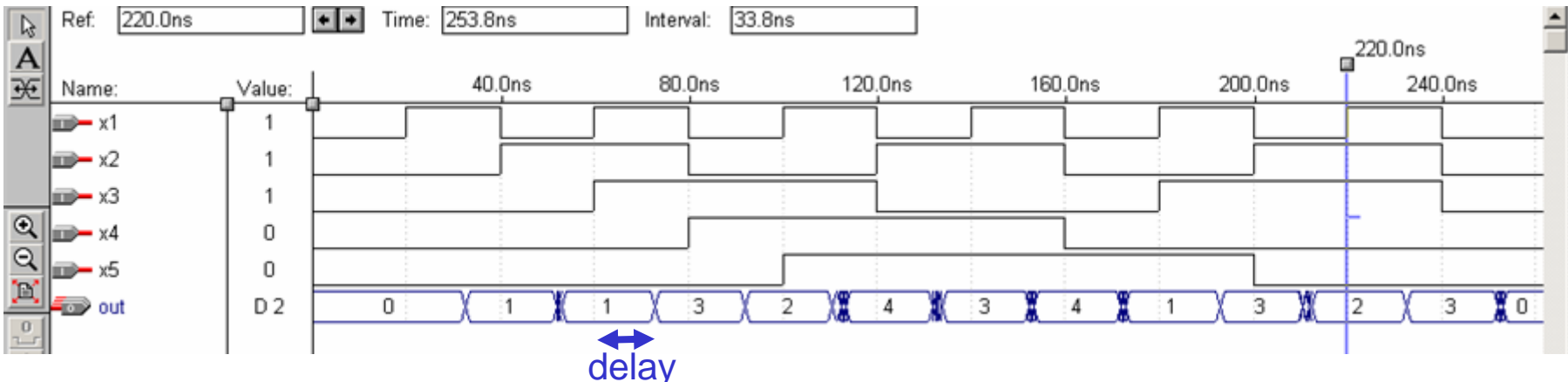 

Unstable output (Delay is 3*kns -- less than Method_1)

Design for Summation Problem (3/7)



Method_3

```
module adder3(x1, x2, x3, x4, x5, clk, out);  
input x1, x2, x3, x4, x5, clk;  
output [2:0] out;  
reg [2:0] out;
```

```
always@(posedge clk)
```

```
out=((x1+x2)+(x3+x4))+x5;
```

```
endmodule
```

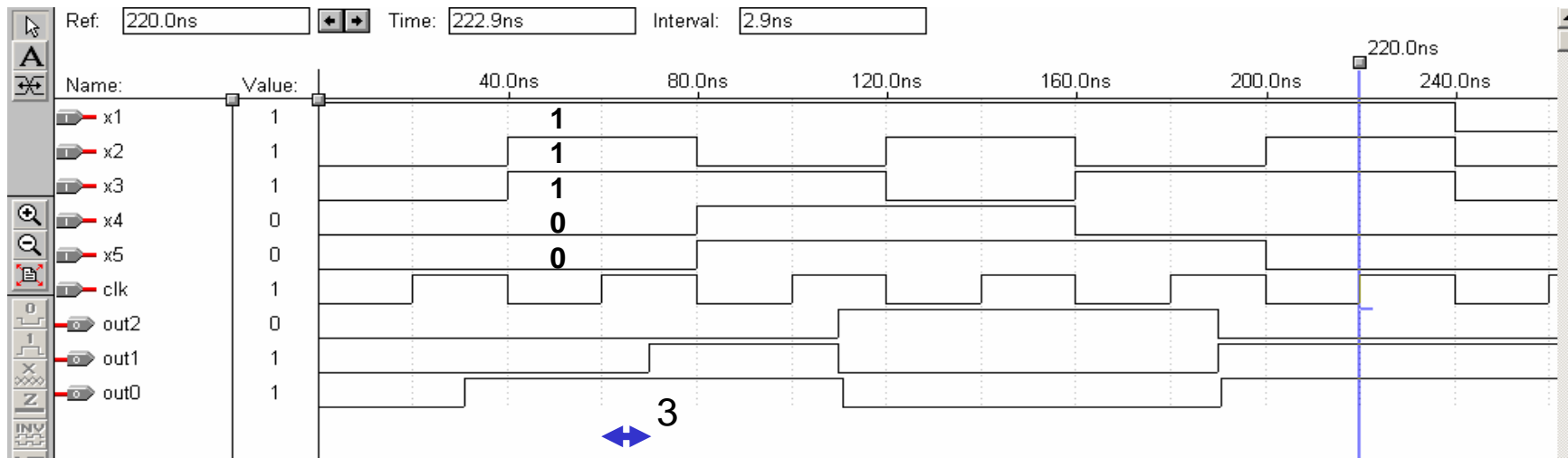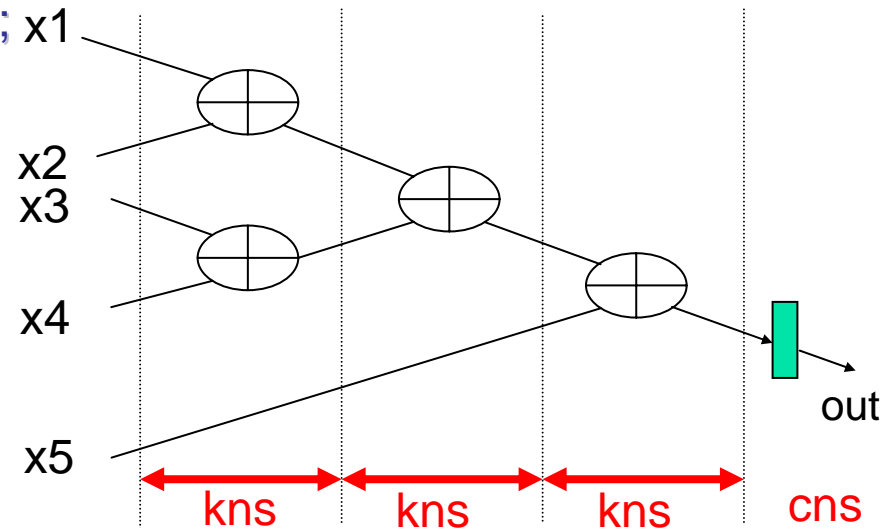


Stable output with register (3-bit flip-flop) Delay is $3 \cdot kns + cns$ (reg assign delay)

Design for Summation Problem (4/7)

Method_4
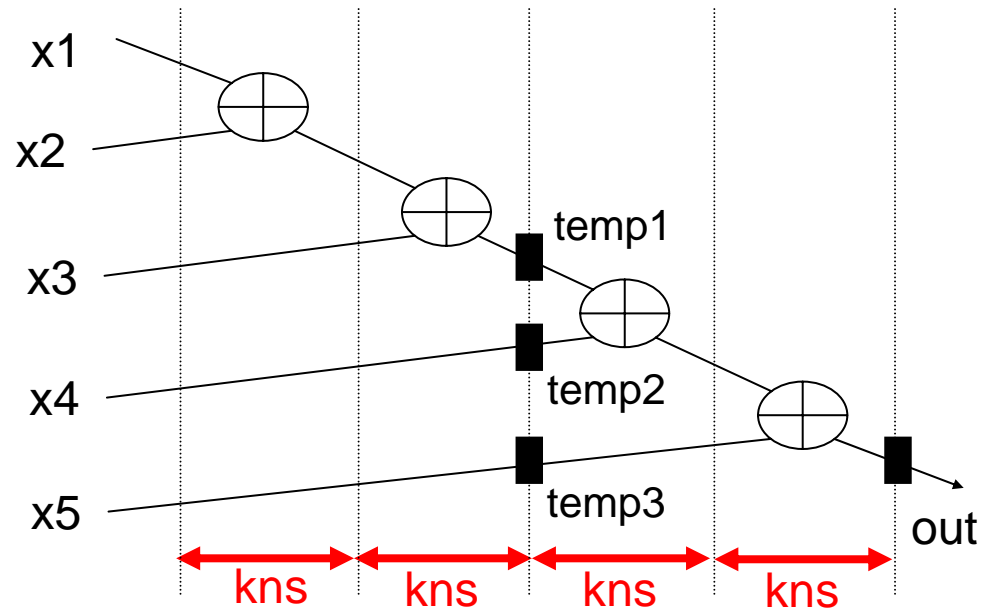
```
module adder4(clk, x1, x2, x3, x4,
x5, out);
input clk,x1, x2, x3, x4, x5;
output [2:0] out;
reg [2:0] out, temp1, temp2,temp3;
always@(posedge clk)
begin
temp1<=(x1+x2)+x3;
temp2<=x4; temp3<=x5;
out<=temp1+temp2+temp3;
end
endmodule
```




Delay is $2 \cdot kns + cns$ which is less than Method_1 ($4kns$), Method_2 ($3kns$) and Method_3 ($3kns + cns$)

So, this method can achieve the best (fastest) clock rate because its critical path is shortest. However, the correct out is generated after two clock cycles not just one (also named as datapath pipelining)

Design for Summation Problem (5/7)

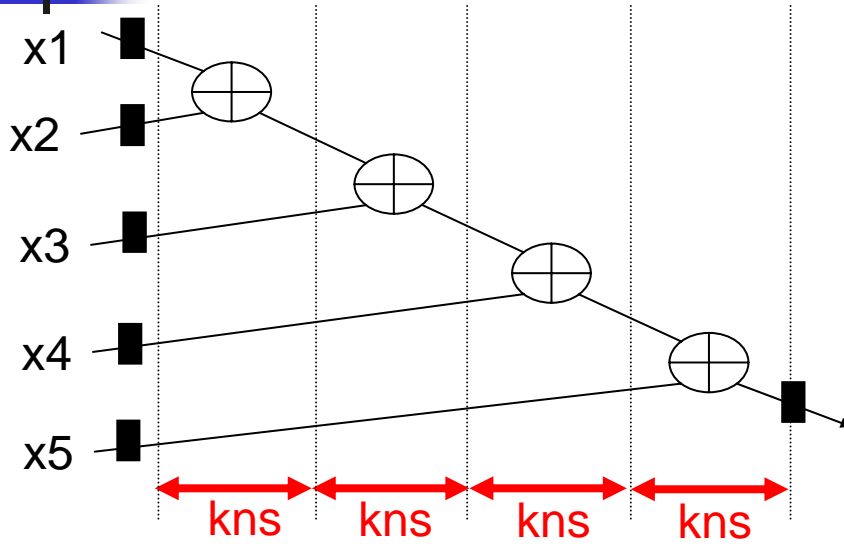
- 1. Wire delay
- 2. Register assignment delay



Critical path is about 4kns

A correct output is generated every clock cycle

Event	1	2	3	4	5	6
Completed time	4k	8k	12k	16k	20k	24k

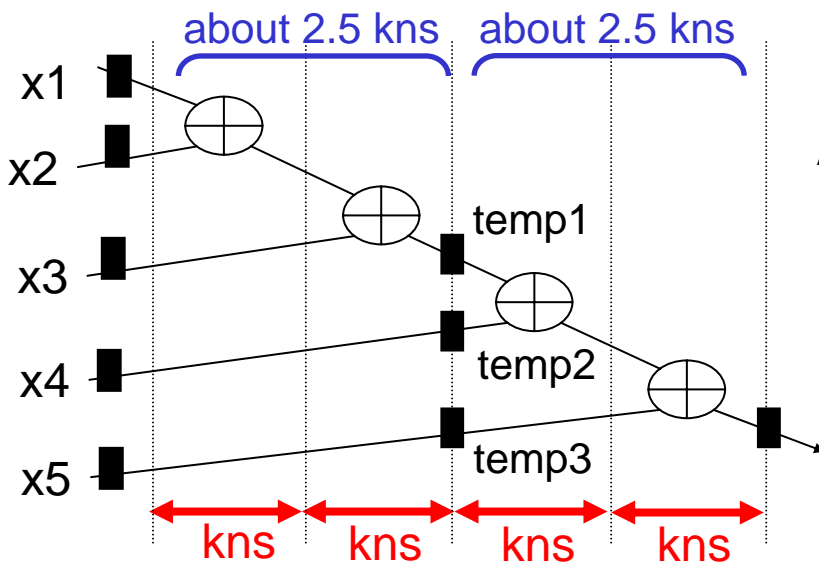

faster clock rate


Critical path is about 2.5kns, why?

A correct output is generated after two clock cycles


Event	1	2	3	4	5	6
Completed time	5k	7.5k	10k	12.5k	15k	17.5k

Two events are parallel processed in the unit.
Faster clock rate but higher cost (3 extra regs)


Design for Summation Problem (6/7)

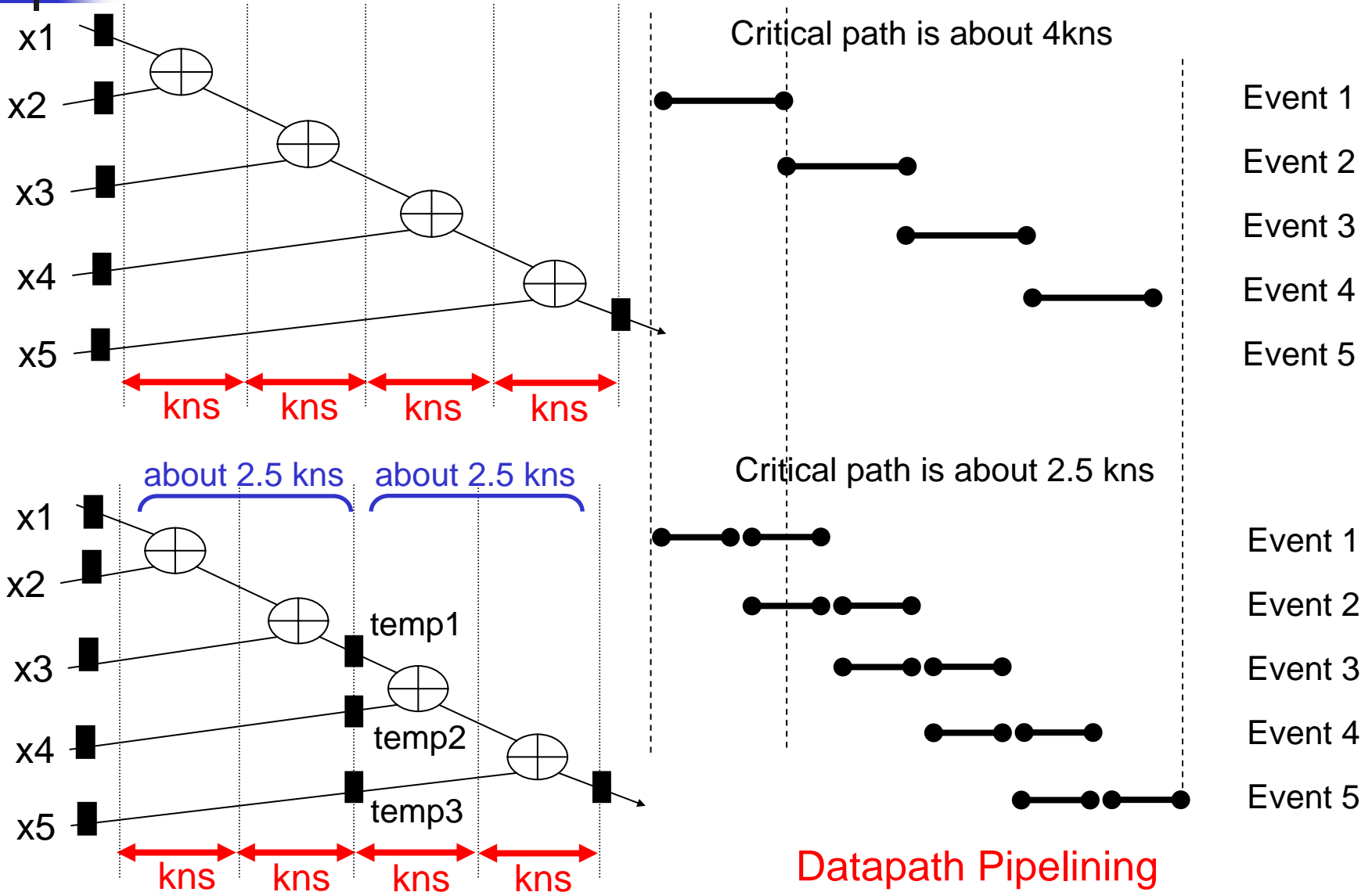

Design for Summation Problem (7/7)

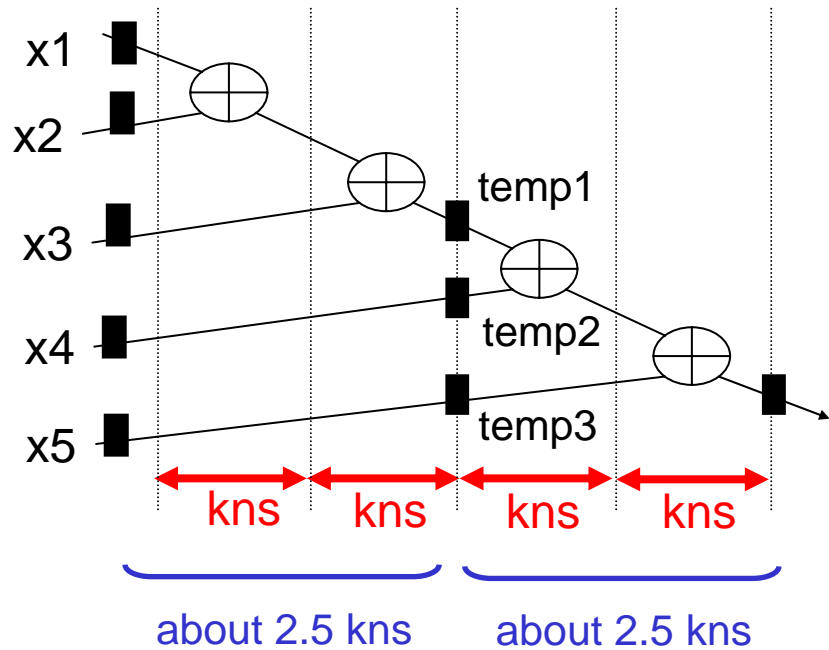


Critical path is about 2.5 kns

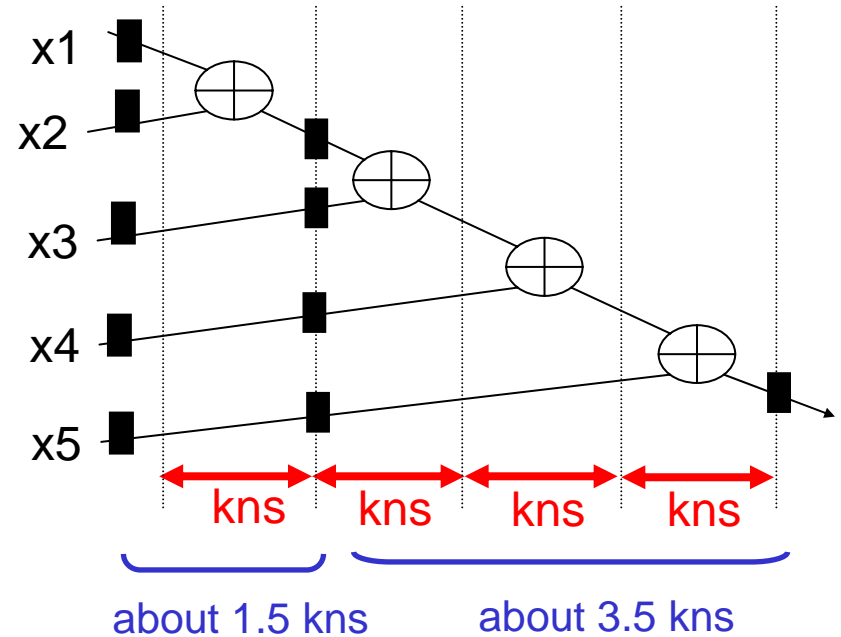

Critical path is about 3.5 kns

Which one is better ? Balance is important

Optimization for RTL Design

 

Optimization for control unit:

1. As suggestion by most textbooks of "Logic System Design"
2. Write a good-style HDL descriptions which are optimized by EDA tools


Optimization for datapath:

1. Resource optimization
2. Time optimization

Control
unit

Optimization for Control Unit

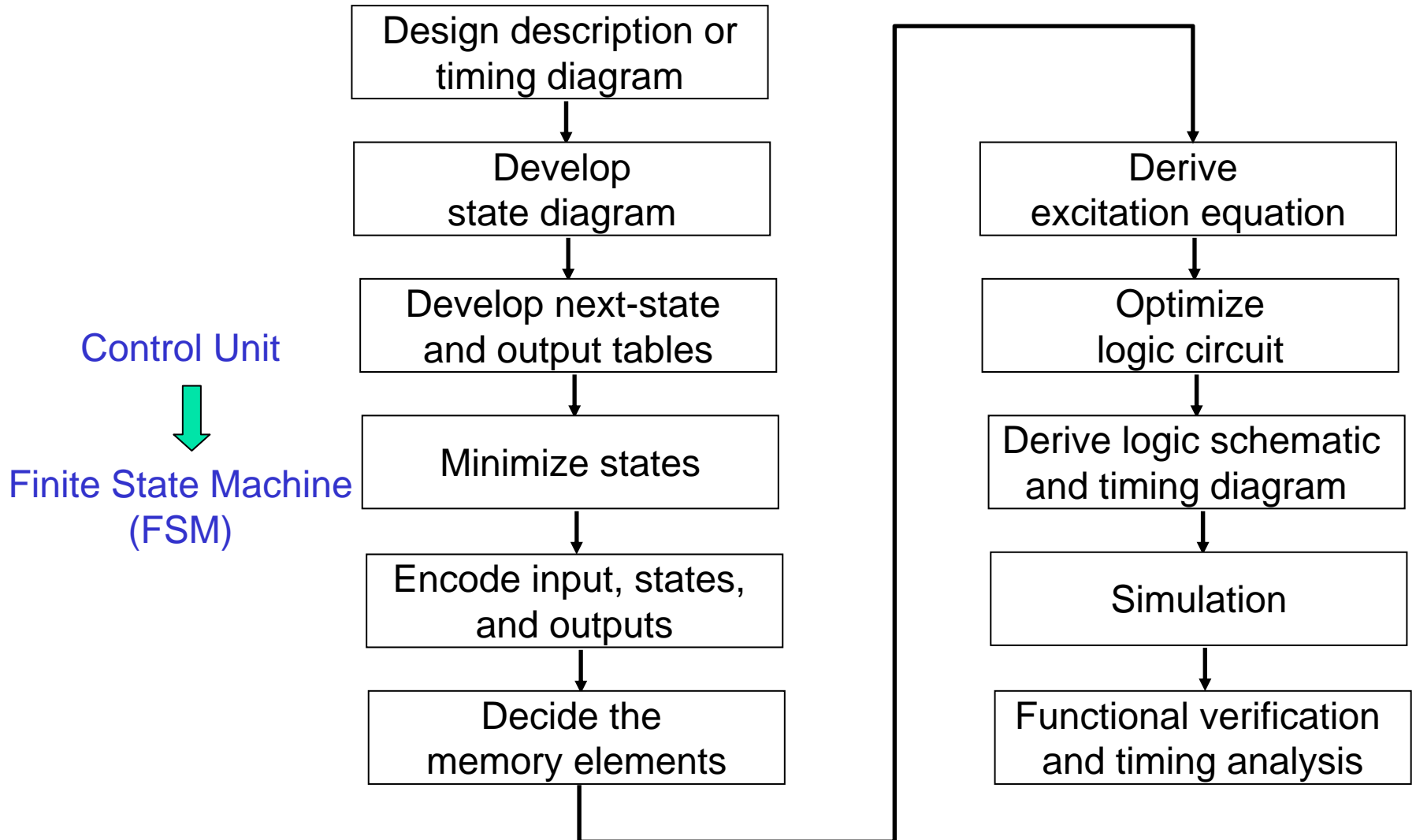Traditional Optimization Flow for Control Unit



Finite State Machine (1/4)


Moore machine: $S \rightarrow O$ (output is dependent only on current state)

Mealy machine: $S \times I \rightarrow O$ (output is dependent on input and state)

State diagram

Four states: S_0, S_1, S_2, S_3

Input/Output

 


Next-state and output tables (I=input)

Present State	Next State		Output	
	I=0	I=1	I=0	I=1
S_0	S_0	S_1	0	1
S_1	S_1	S_2	1	0
S_2	S_2	S_0	0	1
S_3	S_3	S_1	0	1

A mealy machine


Finite State Machine (2/4)

$$S \rightarrow O$$

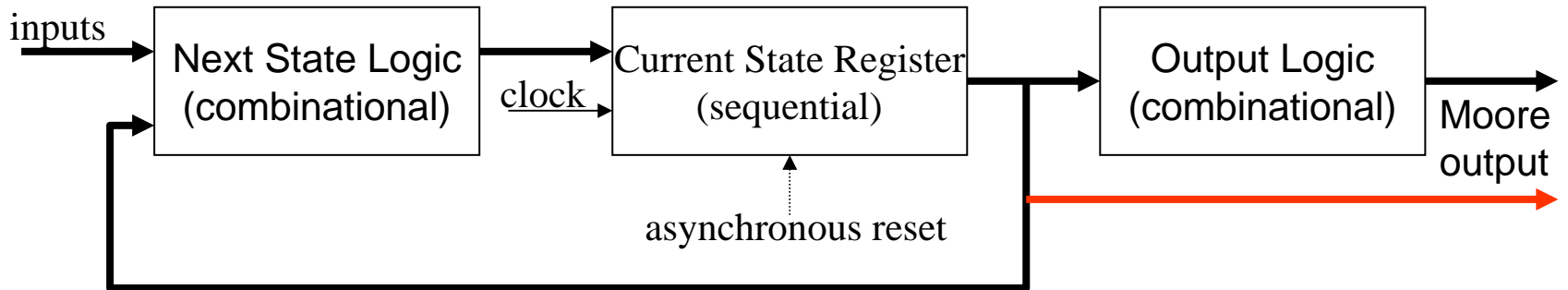

Moore Machine (state-based machine)


$$S \times I \rightarrow O$$

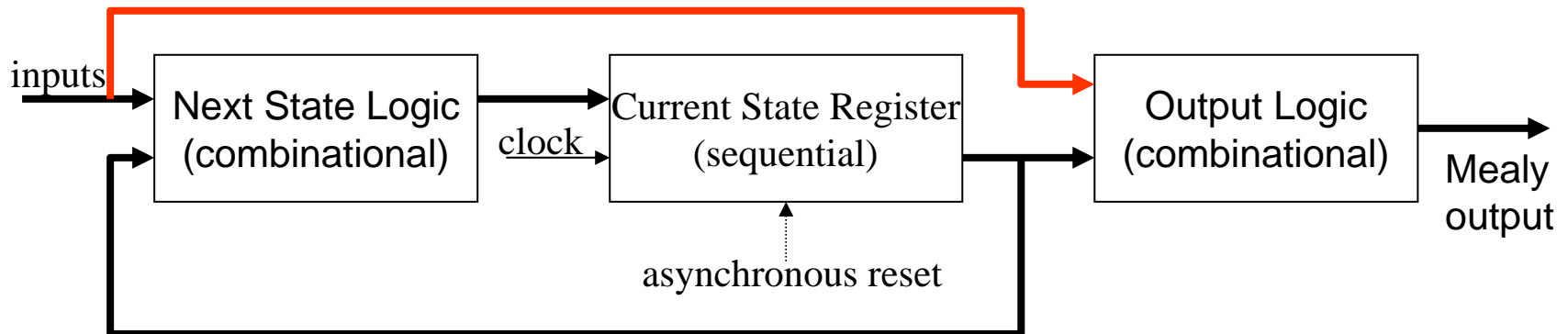

Mealy Machine (input-based machine)

Finite State Machine (3/4)

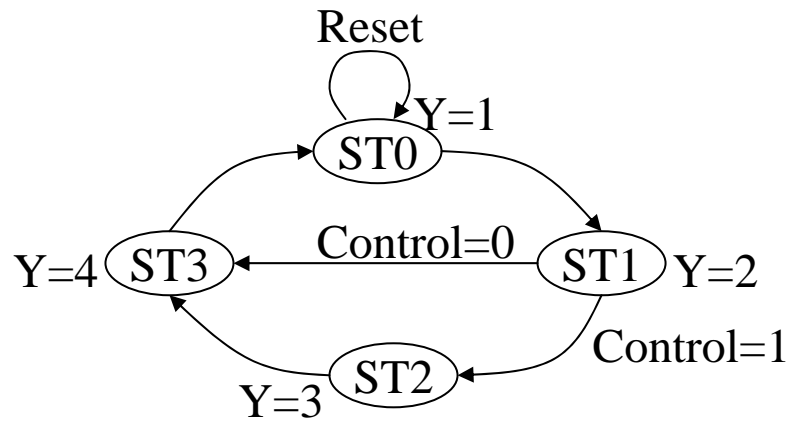- For best legibility, describe FSM using two or three *always@* statements
 - (1) current state or state register (sequential circuit)
 - (2) next state logic (combinational circuit)
 - (3) output logic (combinational circuit)
 - Two combinational logic can be merged
- Use *parameter* to describe the state name



Finite State Machine (4/4)

```
module FSM(Clock, Reset, Control, Y)
input Clock, Reset, Control;
output [2:0] Y;

reg [1:0] CurrentState, Nextstate;
reg [2:0] Y;
```

```
parameter [1:0] ST0 = 2'b00,
                ST1 = 2'b01,
                ST2 = 2'b10,
                ST3 = 2'b11;
```

State name
(parameter)

```
always @(posedge Clock or posedge Reset)
if (Reset)
CurrentState <= ST0;
else
CurrentState <= NextState;
```

State
register
(Seq.C.)

Next state
logic
(Comb.C.)


```
always @(Control or Currentstate)
begin
NextState = ST0;
case (CurrentState)
ST0: NextState <= ST1;
ST1: if (Control)
NextState <= ST2;
else
NextState <= ST3;
ST2: NextState <= ST3;
ST3: NextState <= ST0;
endcase end
```

Output
logic
(Comb.C.)

```
always @(CurrentState)
begin
case(CurrentState)
ST0: Y <= 1; ST1: Y <= 2;
ST2: Y <= 3; ST3: Y <= 4;
endcase
end endmodule
```

Moore Machine (1/8)


Optimization flow

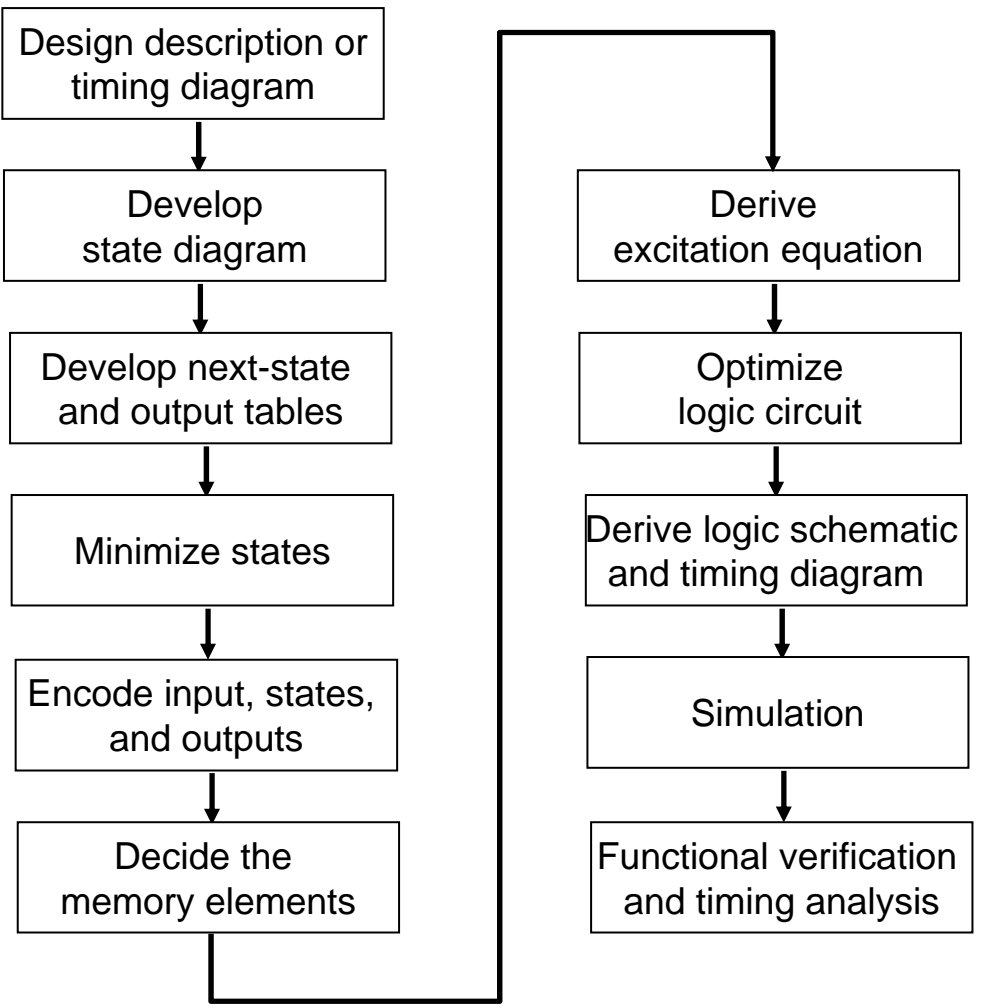

$S \rightarrow O$ S : state O : output

Next-state and output tables (I =input)

Present State	Next State		Output	
	$I=0$	$I=1$	$I=0$	$I=1$
S_0	S_0	S_2	0	0
S_1	S_0	S_2	1	1
S_2	S_2	S_3	1	1
S_3	S_3	S_1	0	0


 


Moore Machine (2/8)

original state table

Present State	Next State		Output	
	I=0	I=1	I=0	I=1
S ₀	S ₀	S ₂	0	0
S ₁	S ₀	S ₂	1	1
S ₂	S ₂	S ₃	1	1
S ₃	S ₃	S ₁	0	0

  Assume that we use JK flip-flops for storage
 4 states \Rightarrow need 2 flip-flops (named M and N)



characteristic table

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

excitation table

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

I	Present State		Next State		M(JK)		N(JK)		Output
	M(t)	N(t)	M(t+1)	N(t+1)	MJ	MK	NJ	NK	
0	0	0	0	0	0	X	0	X	0
1	0	0	1	0	1	X	0	X	0
0	0	1	0	0	0	X	X	1	1
1	0	1	1	0	1	X	X	1	1
0	1	0	1	0	X	0	0	X	1
1	1	0	1	1	X	0	1	X	1
0	1	1	1	1	X	0	X	0	0
1	1	1	0	1	X	1	X	0	0

Moore Machine (3/8)

	MN			
X	00	01	11	10
0	0	0	X	X
1	1	1	X	X

$$MJ=I$$

	MN			
X	00	01	11	10
0	0	X	0	X
1	0	X	1	X

$$NJ=MI$$

	MN			
X	00	01	11	10
0	X	X	0	0
1	X	X	1	0


$$MK=NI$$

	MN			
X	00	01	11	10
0	X	1	0	X
1	X	1	0	X

$$NK=M'$$



	MN			
X	00	01	11	10
0	0	1	0	1
1	0	1	0	1

$$\text{Output} = M'N + MN'$$

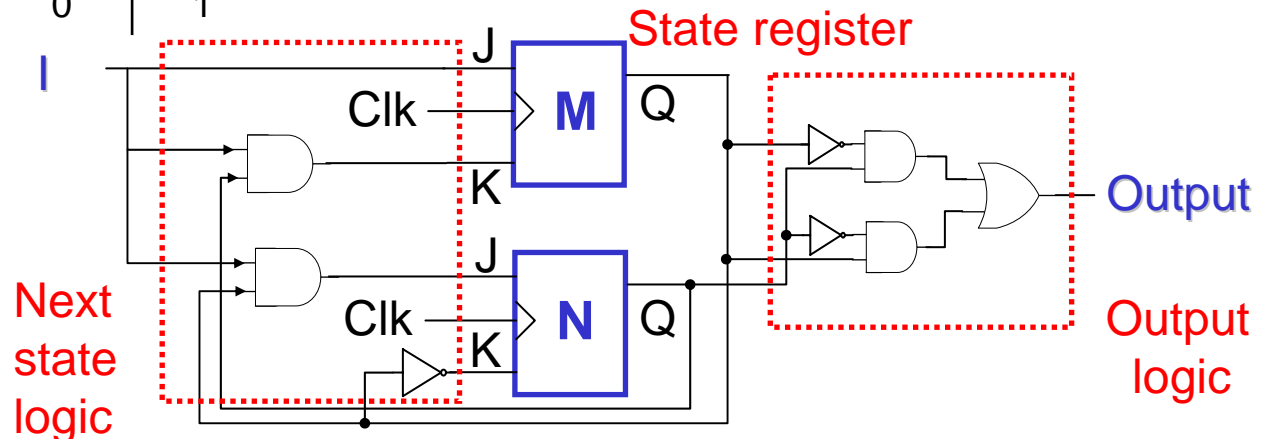


Moore Machine (4/8)

Synthesis Result

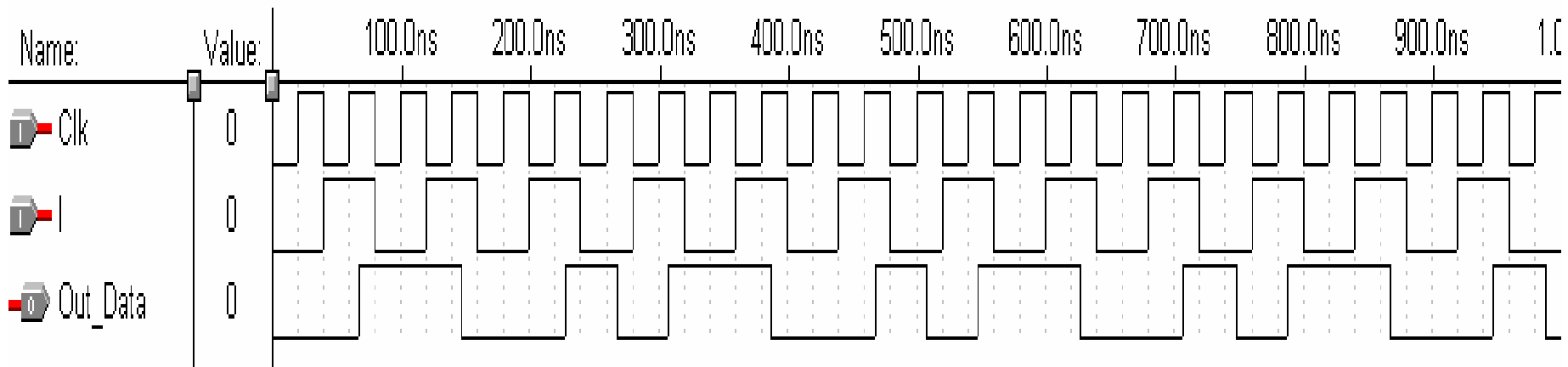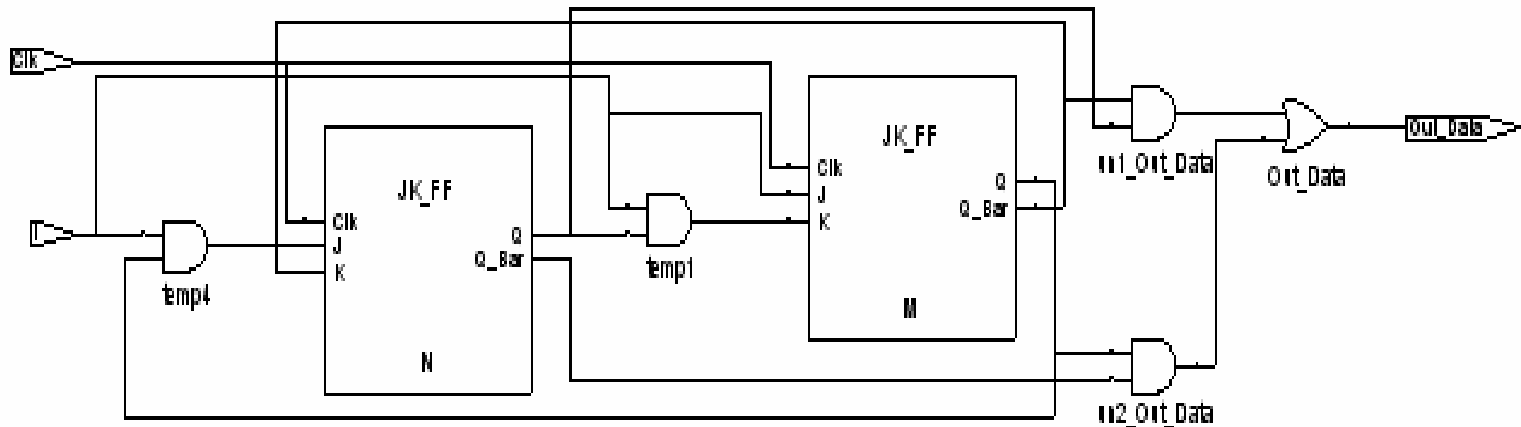

Moore Machine (5/8)

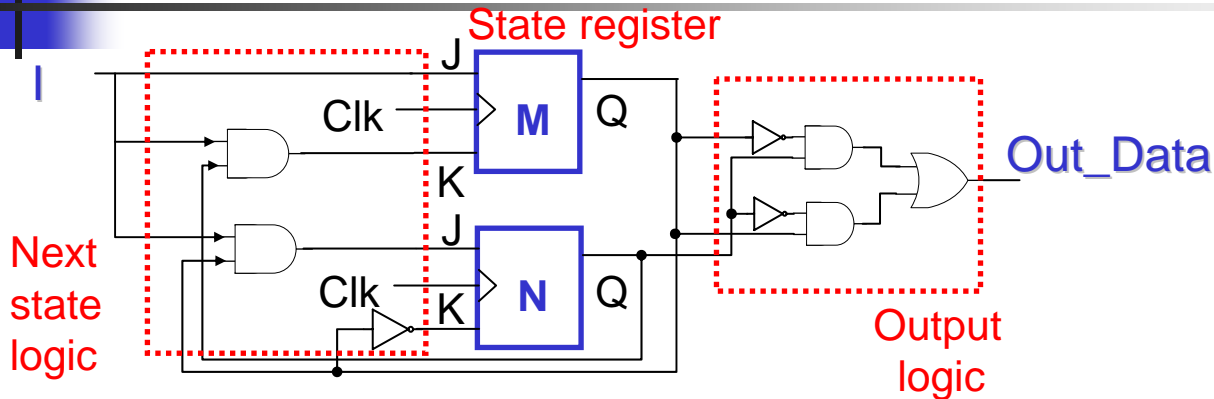

Implement the circuit with structural HDL

```

module moore_JK(Clk, I, Out_Data);
input  Clk, I; output Out_Data;
wire  temp1, temp2, temp3, temp4,
temp5, temp6;
assign temp1 = I & temp5;
assign temp4 = I & temp2;
assign Out_Data = (temp3 &
temp5) | (temp2 & temp6);
JK_FF M(Clk, I, temp1, temp2,
temp3);
JK_FF N(Clk, temp4, temp3, temp5,
temp6);
endmodule

```

```

module JK_FF(Clk, J,
K, Q);
input  Clk, J, K;
output Q, Q_Bar;
reg    Q, Q_Bar;
always @(posedge Clk)
begin
case({J,K})
2'b00:
Q=Q;
2'b01:
Q=0;
2'b10:
Q=1;
2'b11:
Q=~Q;
endcase
end
endmodule

```

Moore Machine-Bad Example (6/8)

The better way is to write behavioral HDL directly and let the EDA tool do the whole optimization job (including Karnaugh Map and logic minimization)

```
module moore_bad(Clk,
Reset, In_Data, Out_Data);
input  Clk, Reset, In_Data;
output [1:0] Out_Data;
reg    [1:0] Out_Data;
reg    [1:0] State;
parameter S0=2'b00,
S1=2'b01, S2=2'b11,
S3=2'b10;
always @(posedge Clk)
begin
    if(Reset)
        State=S0;
    else begin
        case(State)
```

```
    S0: begin
        Out_Data = 0;
        if(In_Data == 1)
            State = S2;
        else
            State = S0;
        end
    S1: begin
        Out_Data = 1;
        if(In_Data == 1)
            State = S2;
        else
            State = S0;
        end
end
```

```
    S2: begin
        Out_Data = 1;
        if(In_Data == 1)
            State = S3;
        else
            State = S2;
        end
    S3: begin
        Out_Data = 0;
        if(In_Data == 1)
            State = S1;
        else
            State = S3;
        end
    endcase
end
end
endmodule
```

Both State and Out_Data are implemented with flip-flops

Note: This is a bad-style HDL

Moore Machine-Good Example (7/8)

```
module moore_good(Clk,  
    Reset, In_Data, Out_Data);
```

```
input Clk, Reset, In_Data;  
output [1:0] Out_Data;  
reg [1:0] Out_Data;  
reg [1:0] State, NextState;  
parameter S0=2'b00, S1=2'b01,  
    S2=2'b10, S3=2'b11;
```

```
always @(posedge Clk or  
    posedge Reset)
```

```
begin  
    if(Reset)  
        State = S0;  
    else  
        State = NextState;  
end
```

State register (flip-flops)

```
always @(In_Data or State)  
begin
```

```
    case(State)  
        S0: begin  
            if(In_Data == 1)  
                NextState = S2;  
            else  
                NextState = S0;  
        end
```

```
        S1: begin  
            if(In_Data == 1)  
                NextState = S2;  
            else  
                NextState = S0;  
        end
```

```
        S2: begin  
            if(In_Data == 1)  
                NextState = S3;  
            else  
                NextState = S2;  
        end
```

```
        S3: begin  
            if(In_Data == 1)  
                NextState = S1;  
            else  
                NextState = S3;  
        end  
    endcase  
end
```

Next state logic

```
always @(State)  
begin
```



```
    case(State)  
        S0: Out_Data = 0;  
        S1: Out_Data = 1;  
        S2: Out_Data = 1;  
        S3: Out_Data = 0;  
    endcase
```

```
end  
endmodule
```

Output logic

Note: This is a good-style HDL (only "State" is implemented with flip-flops)

Moore Machine-Good Example (8/8)

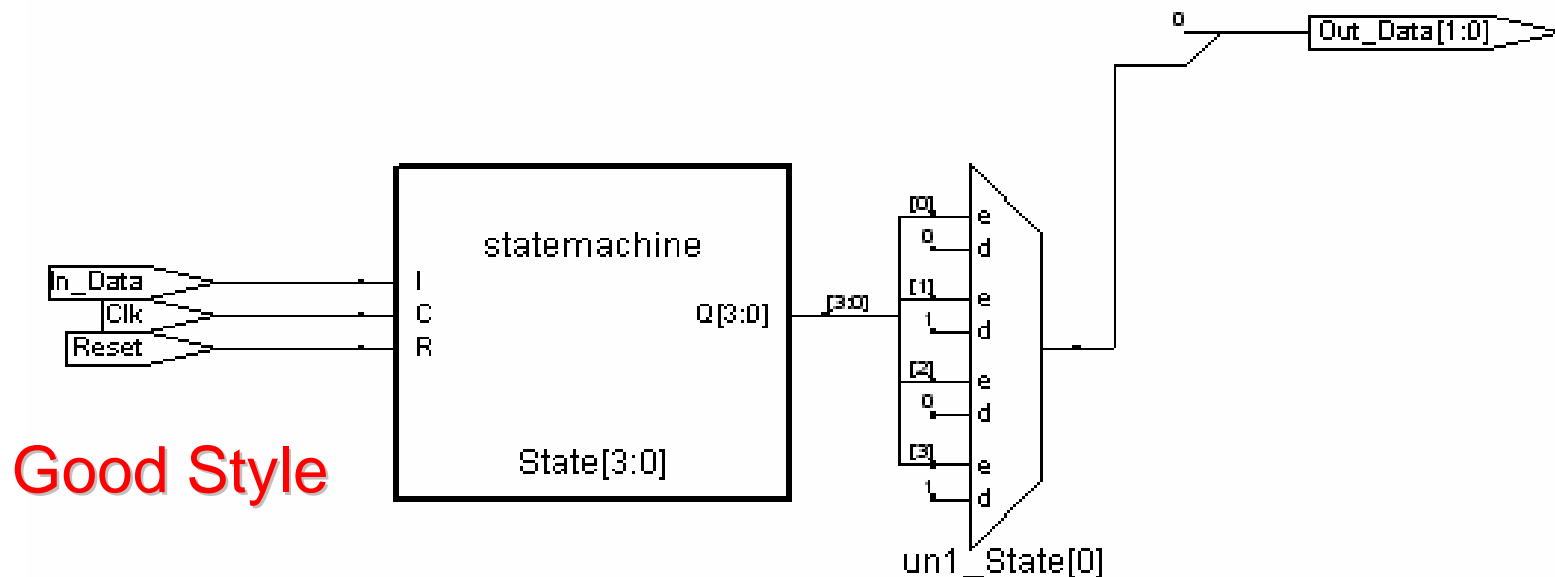 


Mealy Machine (1/2)

State diagram

Four states: S_0, S_1, S_2, S_3

Input/Output

 


Next-state and output tables (I=input)

Present State	Next State		Output	
	I=0	I=1	I=0	I=1
S_0	S_0	S_1	0	1
S_1	S_1	S_2	1	0
S_2	S_2	S_0	0	1
S_3	S_3	S_1	0	1

Mealy Machine (2/2)

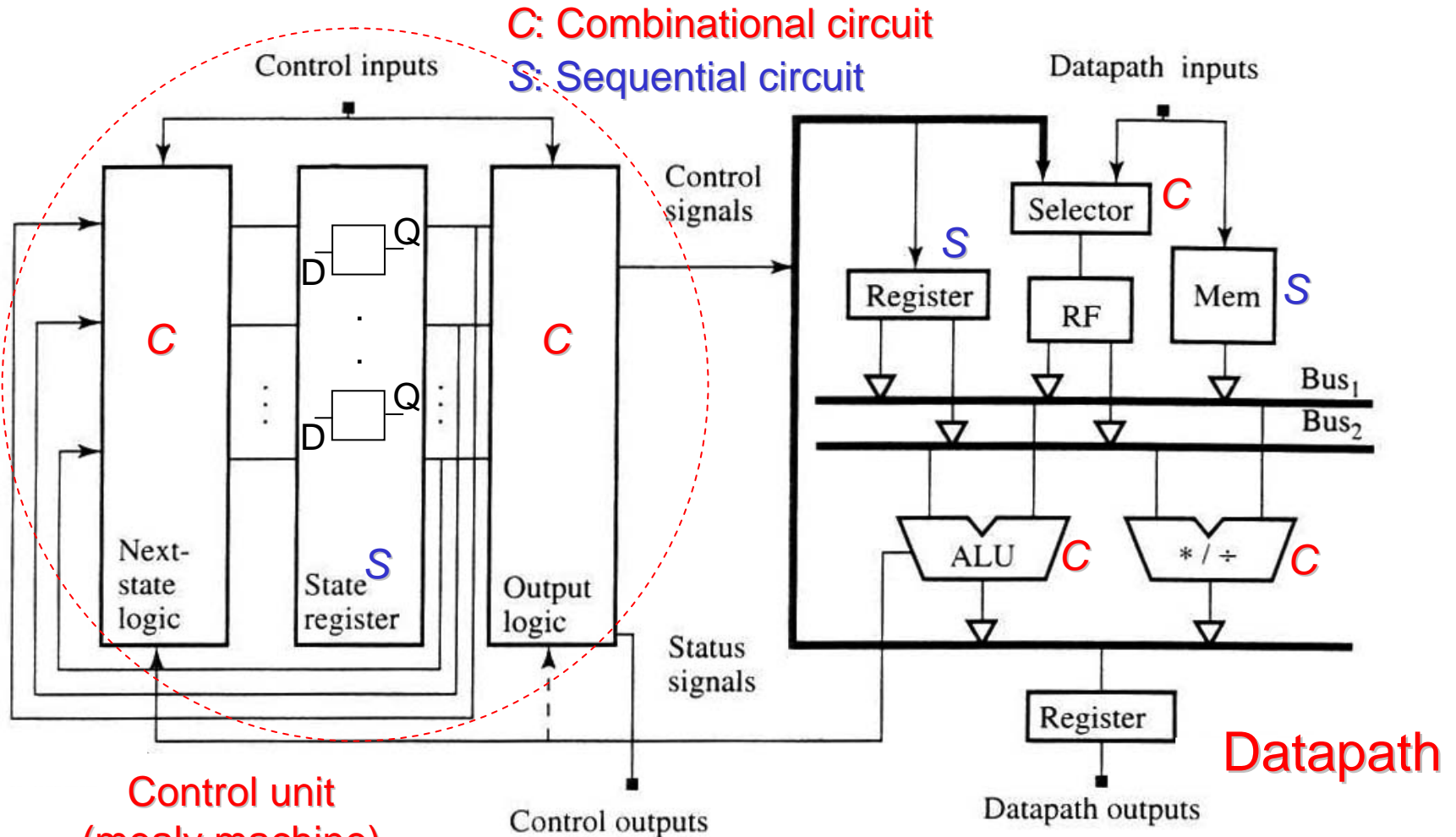Please do remember to write your mealy machine by using the good-style HDL




Control unit
(mealy machine)

Using three always statements

Homework: implement a mealy machine


Control-Unit Implementation Styles (1/3)

Hardwired
Control

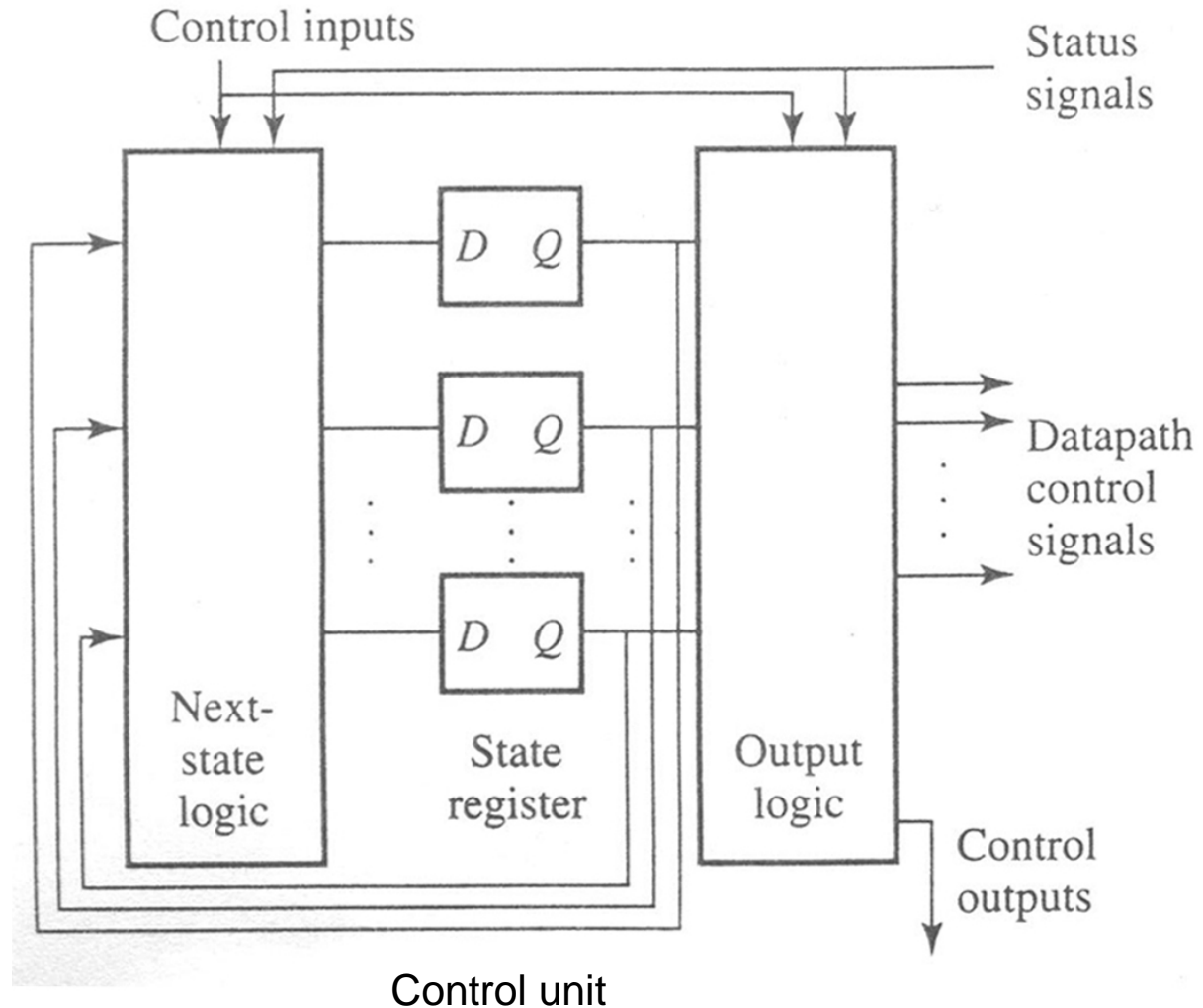

Control-Unit Implementation Styles (2/3)


Hardwired
Control

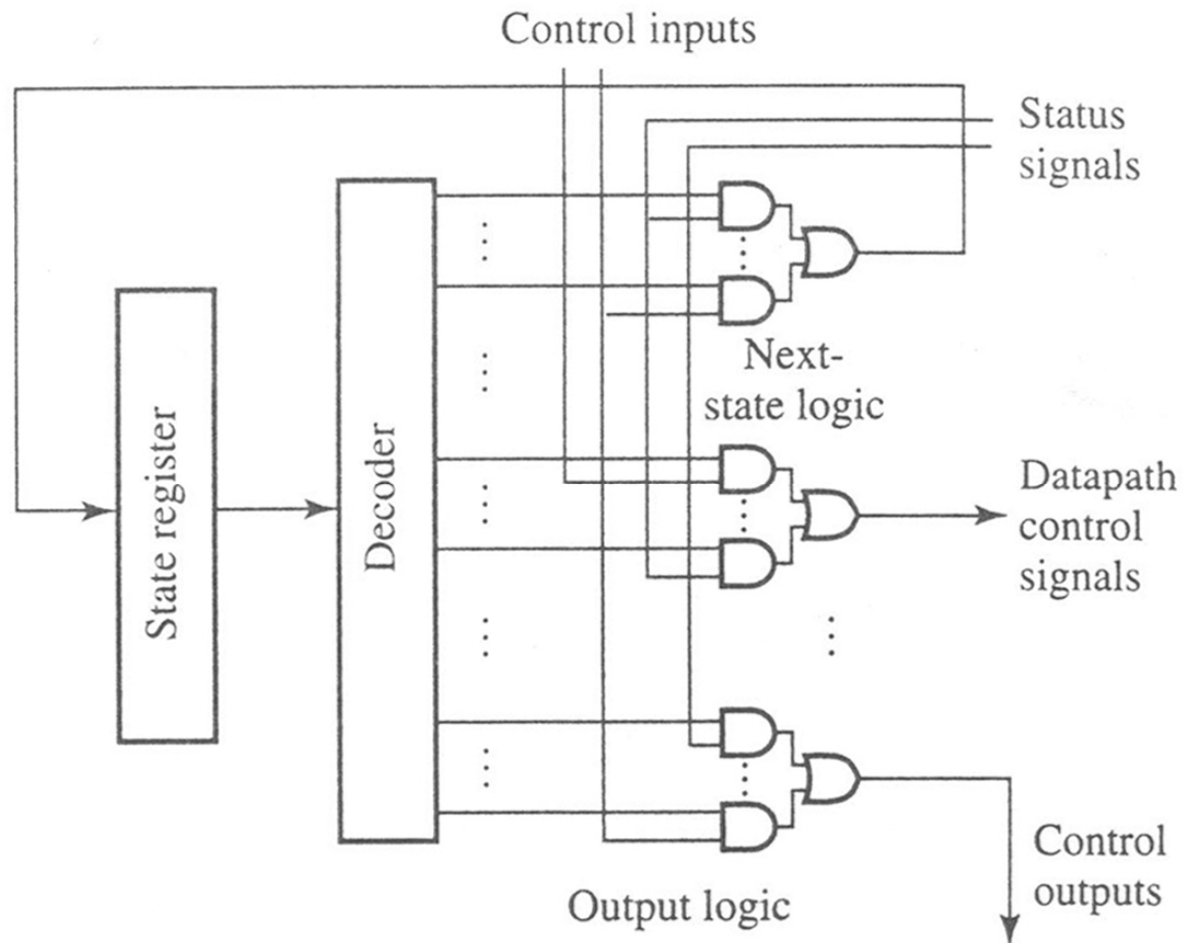

Control unit with state-register and decoder

Control-Unit Implementation Styles (3/3)

Microprogramming Control

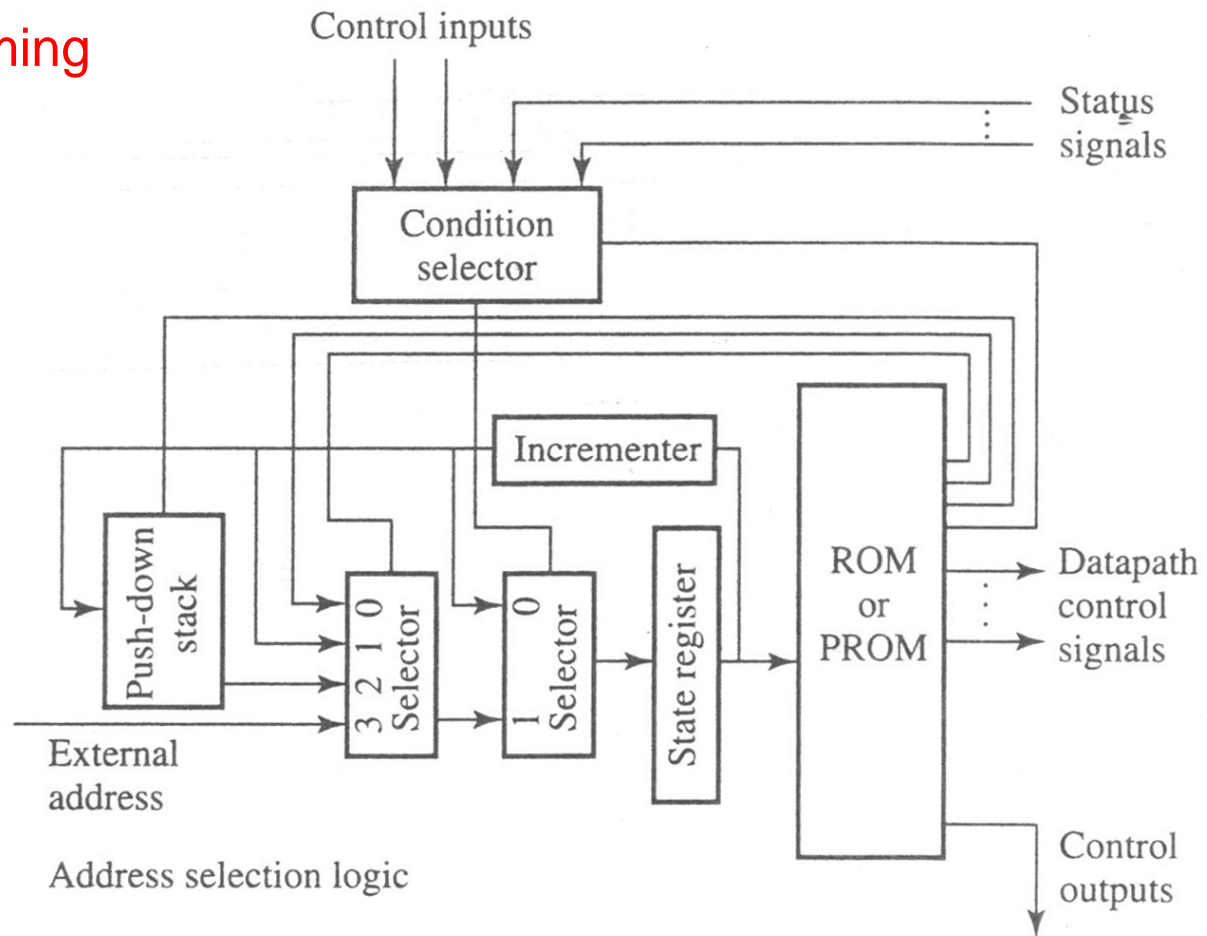

Control unit with state-register and ROM



One's Count Problem (1/2)

One's – counter implementation

Problem : Using a datapath with a 3 port register-file (2 read port and 1 write port), design a one's counter that count the number of ones in an input dataword, and return the result after completion

Data := Input

Ocount := 0

Mask := 1

while Data \neq 0 **repeat**


Temp := Data AND Mask

Ocount := Ocount + Temp



Data := Data >> 1

end while


Outport := Ocount

 

One's count Problem (2/2)

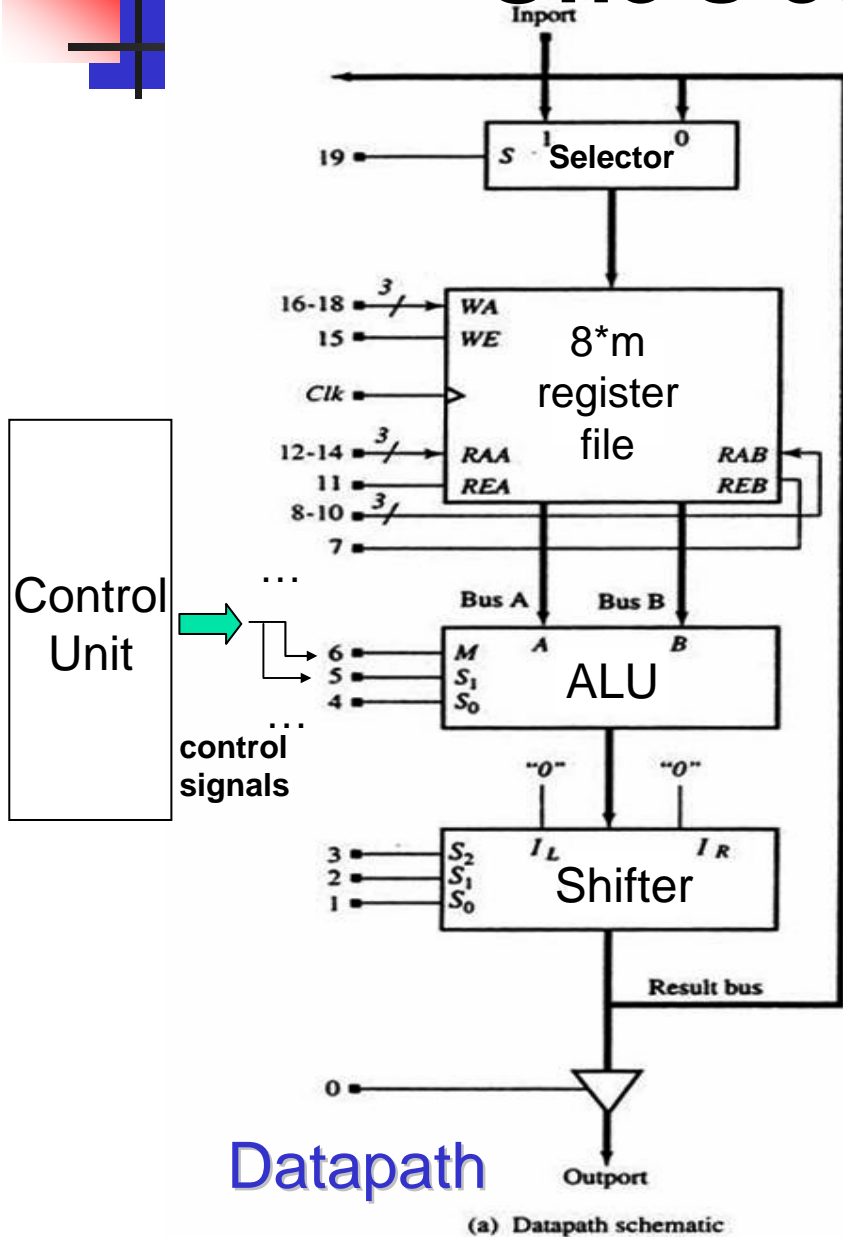 

(a) Datapath schematic

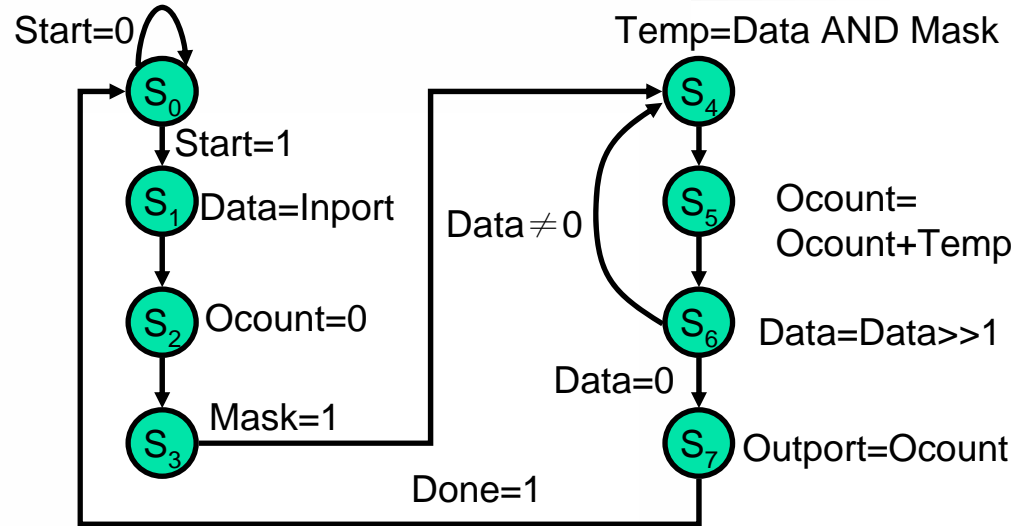

	IE	WT AD	READ AD A	READ AD B	ALU	SHIFT	O E
1	1	R ₁	X	X	X	X	0
2	0	R ₃	0	0	Add	Pass	0
3	0	R ₂	0	X	Inc	Pass	0
4	0	R ₄	R ₁	R ₂	AND	Pass	0
5	0	R ₃	R ₃	R ₄	Add	Pass	0
6	0	R ₁	R ₁	0	Add	Shift right	0
7	0	None	R ₃	0	Add	Pass	1



Datapath of One's-Counter (1/4)

Optimized by EDA tool

```
module data_path(clock,reset,control_word,inport,outport,data);
input clock,reset;
input [19:0] control_word;
input [7:0] inport;
output [7:0] outport,data;
wire [7:0] line1,line2,line3,line4;

selector O1(.inp_A(inport), .inp_B(data), .select(control_word[19]), .outp(line1));

register NO2(.clock(clock), .reset(reset), .WA(control_word[17:15]),
.WE(control_word[18]), .RAA(control_word[13:11]), .REA(control_word[14]),
.RAB(control_word[9:7]), .REB(control_word[10]), .Data_in(line1), .Bus_A(line2),
.Bus_B(line3));

alu NO3(.Datain_A(line2), .Datain_B(line3), .select(control_word[6:4]), .outp(line4));

shifter NO4(.inp(line4), .select(control_word[3:1]), .outp(data));

buffer NO5(.OE(control_word[0]), .inp(data), .outp(outport));
endmodule
```

Datapath of One's-Counter (2/4)

```

module selector(inp_A,inp_B,select,outh);
input  [7:0] inp_A,inp_B;
input  select;
output [7:0] outh;
reg    [7:0] outh;

```

```

always@(select or inp_A or inp_B)
begin
    if(select)
        outh = inp_A;
    else
        outh = inp_B;
end
endmodule

```

M	S ₁	S ₀	ALU OPERATIONS
0	0	0	Complement A
0	0	1	AND
0	1	0	EX-OR
0	1	1	OR
1	0	0	Decrement A
1	0	1	Add
1	1	0	Subtract
1	1	1	Increment A

```

module alu(Datain_A,Datain_B,select,outh);
input  [7:0] Datain_A,Datain_B;
input  [2:0] select;
output [7:0] outh; reg    [7:0] outh;

```

```

always@(select or Datain_A or Datain_B)
begin
    case(select)
        3'b000:outh = ~Datain_A;
        3'b001:outh = Datain_A & Datain_B;
        3'b010:outh = Datain_A ^ Datain_B;
        3'b011:outh = Datain_A | Datain_B;
        3'b100:outh = Datain_A - 1;
        3'b101:outh = Datain_A + Datain_B;
        3'b110:outh = Datain_A - Datain_B;
        3'b111:outh = Datain_A + 1;
    endcase
end
endmodule

```

Datapath of One's-Counter (3/4)

```

module shifter(inp,select,outp);
input [7:0] inp;
input [2:0] select;
output [7:0] outp;
reg [7:0] outp;
reg temp;
always@(select or inp)
begin
    case(select)
        3'b000:outp = inp;
        3'b001:outp = inp;
        3'b100:outp = inp << 1;
        3'b101:
            begin
                temp = inp[7];
                outp = inp << 1;
                outp[0] = temp;
            end
        3'b110:outp = inp >> 1;
    endcase
end

```

```

3'b111:
begin
    temp = inp[0]; outp = inp >> 1;
    outp[7] = temp;
end
default: outp=8'hxx;
endcase
end
endmodule

module buffer(OE,inp,outp);
input OE;
input [7:0] inp;
output [7:0] outp;
reg [7:0] outp;
always@(OE or inp)
begin
    if(OE)
        outp = inp;
    else outp=8'bz;
end
endmodule

```

S ₂	S ₁	S ₀	SHIFT OPERATIONS
0	0	0	Pass
0	0	1	Pass
0	1	0	Not used
0	1	1	Not used
1	0	0	Shift left
1	0	1	Rotate left
1	1	0	Shift right
1	1	1	Rotate right



Datapath of One's-Counter (4/4)

```
module  register(clock,reset,WA,WE,RAA,
  REA,RAB,REB,Data_in,Bus_A,Bus_B);
input   clock,reset,WE,REA,REB;
input   [2:0] WA,RAA,RAB;
input   [7:0] Data_in; output [7:0] Bus_A,Bus_B;
reg [7:0] reg_array [7:0];


always@(posedge clock)
begin
  if(reset)
    begin
      reg_array[0]=8'h00; reg_array[1]=8'h00;
      reg_array[2]=8'h00; reg_array[3]=8'h00;
      reg_array[4]=8'h00; reg_array[5]=8'h00;
      reg_array[6]=8'h00; reg_array[7]=8'h00; end
    else
      begin
        if(WE)
          reg_array[WA]=Data_in;
        end
      end
end
end

assign Bus_A=REA?reg_array[RAA]:8'h00;
assign Bus_B=REB?reg_array[RAB]:8'h00;
endmodule
```

Controller of One's-Counter (1/8)


- State lasts for a clock cycle
- In each state the datapath executes the statement indicated on its right side.
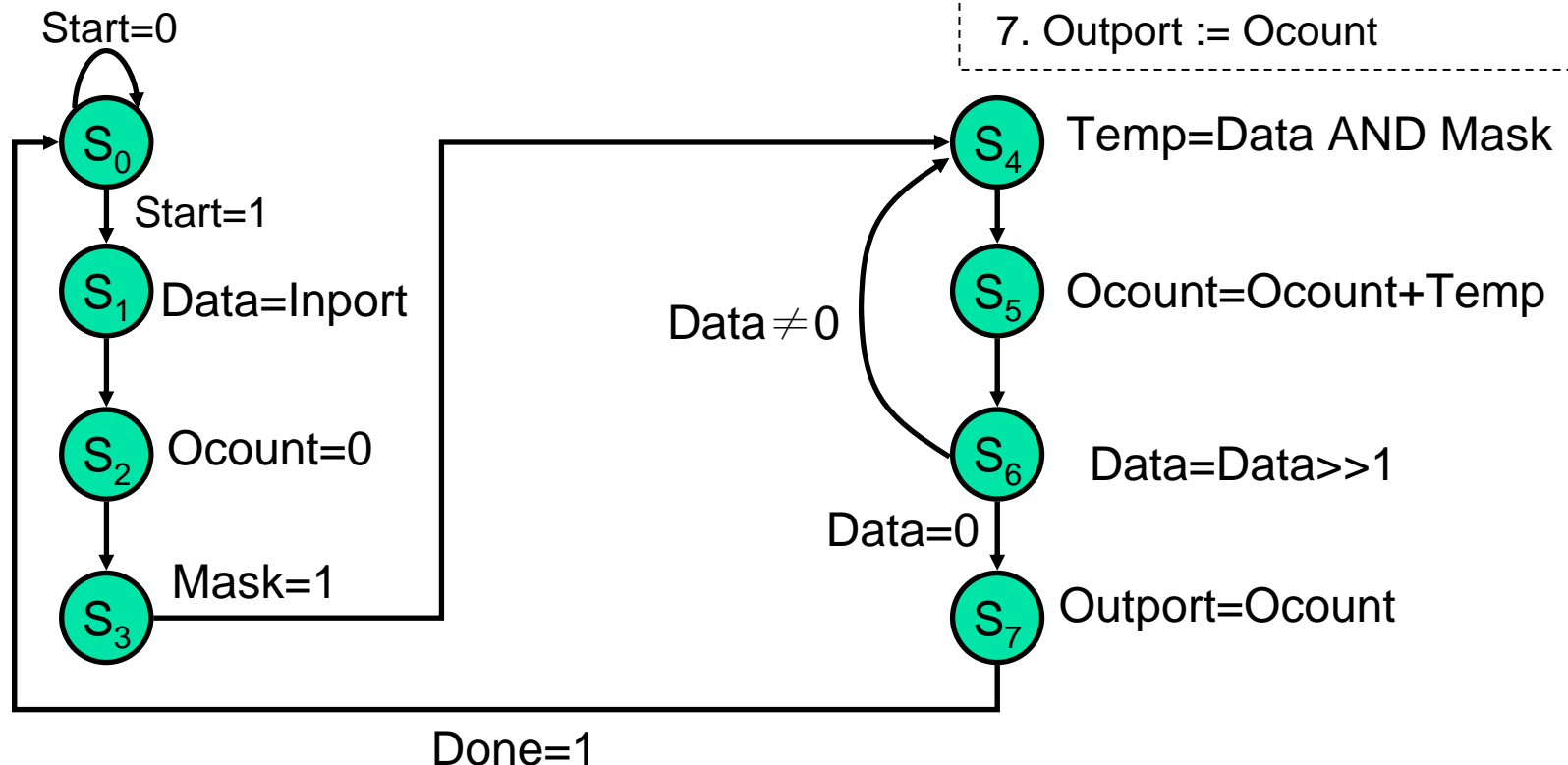
```
1. Data := Input
2. Ocount := 0
3. Mask := 1
   while Data ≠ 0 repeat
4. Temp := Data AND Mask
5. Ocount := Ocount + Temp
6. Data := Data >> 1
   end while
7. Output := Ocount
```



Controller of One's-Counter (2/8)

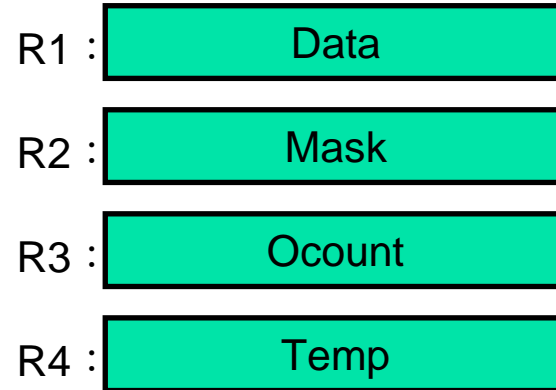1. Data := Input
2. Ocount := 0
3. Mask := 1
- while** Data :=≠ 0 **repeat**
4. Temp := Data AND Mask
5. Ocount := Ocount + Temp
6. Data := Data >> 1
- end while**
7. Outport := Ocount



Control words for one's counter

Control WORDS	IE	WRITE ADDRESS	READ ADDRESS A	READ ADDRESS B	ALU OPERATION	SHIFTER OPERATION	OE
1	1	R ₁	X	X	X	X	0
2	0	R ₃	0	0	Add	Pass	0
3	0	R ₂	0	X	Increment	Pass	0
4	0	R ₄	R ₁	R ₂	AND	Pass	0
5	0	R ₃	R ₃	R ₄	Add	Pass	0
6	0	R ₁	R ₁	0	Add	Shift right	0
7	0	None	R ₃	0	Add	Pass	1

← word

Controller of One's-Counter (3/8)

State	$Q_2 Q_1 Q_0$	IE	Write address				Read address A				Read address B				ALU operations			Shift operations			OE
			WE	WA ₂	WA ₁	WA ₀	REA	RAA ₂	RAA ₁	RAA ₀	REB	RAB ₂	RAB ₁	RAB ₀	M	S ₁	S ₀	S ₂	S ₁	S ₀	
s ₀	000	0	0	X	X	X	0	X	X	X	0	X	X	X	X	X	X	X	X	X	0
s ₁	001	1	1	0	0	1	0	X	X	X	0	X	X	X	X	X	X	X	X	X	0
s ₂	010	0	1	0	1	1	0	X	X	X	0	X	X	X	1	0	1	0	0	0	0
s ₃	011	0	1	0	1	0	0	X	X	X	0	X	X	X	1	1	1	0	0	0	0
s ₄	100	0	1	1	0	0	1	0	0	1	1	0	1	0	0	1	0	0	0	0	0
s ₅	101	0	1	0	1	1	1	0	1	1	1	0	0	1	0	1	0	0	0	0	0
s ₆	110	0	1	0	0	1	1	0	0	1	0	X	X	X	1	0	1	1	1	0	0
s ₇	111	0	0	X	X	X	1	0	1	1	0	X	X	X	1	0	1	0	0	0	1

(a) Output logic table

Optimized by hand

$$IE = Q_2' Q_1' Q_0$$

$$WA_2 = Q_1' Q_0'$$

$$WA_1 = Q_2 Q_0 + Q_2' Q_1$$

$$WA_0 = Q_1' Q_0 + Q_1 Q_0'$$

$$WE = Q_2 Q_1' + Q_2' Q_0 + Q_1 Q_0'$$

$$RAB_2 = Q_0$$

$$RAB_1 = Q_0'$$

$$RAB_0 = 0$$

$$REB = Q_2 Q_1'$$

$$RAB_2 = Q_0$$

$$RAB_1 = Q_0'$$

$$RAB_0 = 0$$

$$REB = Q_2 Q_1'$$

$$M = Q_1 + Q_0$$

$$S_1 = Q_2' Q_0$$

$$S_0 = 1$$

$$S_2 = S_1 = Q_2 Q_1' Q_0'$$

$$S_0 = 0$$

$$OE = Q_2 + Q_1 + Q_0$$

(b) Output equations

Controller of One's-Counter (4/8)

Start .(Data ≠ 0)

States	$Q_2Q_1Q_0$	00	01	10	11
S_0	000	000	000	001	001
S_1	001	010	010	010	010
S_2	010	011	011	011	011
S_3	011	100	100	100	100
S_4	100	101	101	101	101
S_5	101	110	110	110	110
S_6	110	100	111	100	111
S_7	111	000	000	000	000

(a) Next-state table

Start	Q_1Q_0	$Q_2=0$				$Q_2=1$			
		00	01	11	10	00	01	11	10
Data ≠ 0	00	000	010	100	011	101	110	000	100
	01	000	010	100	011	101	110	000	111
	11	001	010	100	011	101	110	000	111
	10	001	010	100	011	101	110	000	100

(b) Karnaugh map

Optimized by hand


$$Q_2(\text{next}) = Q'_2Q_1Q_0 + Q_2Q'_1 + (\text{Data} \neq 0)Q_2Q'_0$$

$$Q_1(\text{next}) = Q'_1Q_0 + Q'_2Q'_1Q'_0 + (\text{Data} \neq 0)Q_1Q'_0$$

$$Q_0(\text{next}) = Q'_2Q_1Q'_0 + \text{Start} Q'_2Q'_0 + (\text{Data} \neq 0)Q_2Q'_0$$

(c) Next-state equations

Controller of One's-Counter (5/8)

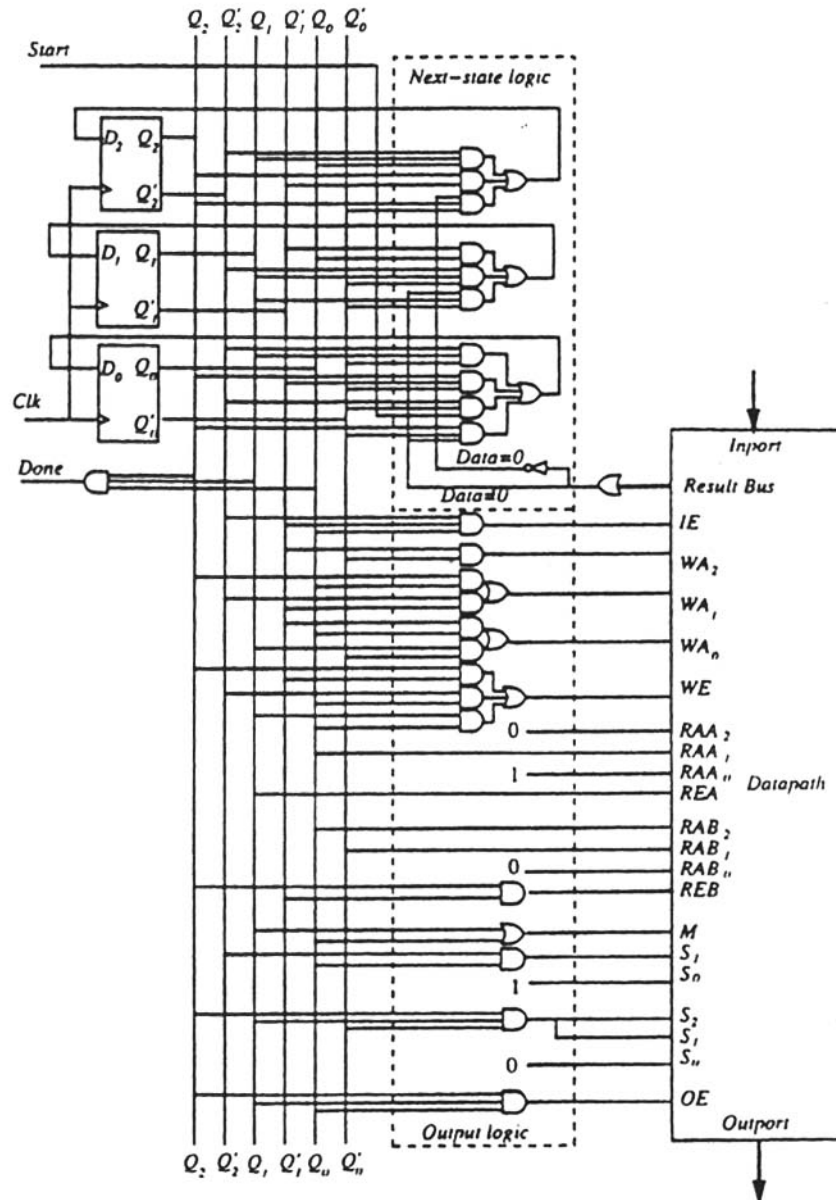

Optimized by hand

Controller of One's-Counter (6/8)

```
module one_counter(clock,reset,start,inport,done,output);
input  clock,reset,start; input  [7:0] inport;
output done; output  [7:0] output;
wire  [7:0] data; wire  [19:0] control_word;
control_unit NO1(.clock(clock), .reset(reset), .start(start), .data(data),
                .control_word(control_word), .done(done));
data_path NO2(.clock(clock), .reset(reset), .control_word(control_word),
              .inport(inport), .outport(output), .data(data));
endmodule
```

Optimized by EDA tool

```
module control_unit(clock,reset,start,data,control_word,done);
input  clock,reset,start; input  [7:0] data;
output done; output  [19:0] control_word;
parameter S0=0,S1=1,S2=2,S3=3,S4=4,S5=5,S6=6,S7=7;
reg    [2:0] currentstate,nextstate;
reg    done; reg    [19:0] control_word;
```

```
always@(posedge clock)
```

```
begin
```

```
  if(reset)
```

```
    currentstate=S0;
```

```
  else
```

```
    currentstate=nextstate;
```

```
end
```

*State Register
(Seq. C.)*

Controller of One's-Counter (7/8)

Next State Logic (Comb. C.)

```
always@(currentstate or start or data)
```

```
begin
```

```
  case(currentstate)
```

```
    S0:
```

```
      begin
```

```
        if(start==0)
```

```
          nextstate=S0;
```

```
        else
```

```
          nextstate=S1;
```

```
      end
```

```
    S1:
```

```
      nextstate=S2;
```

```
    S2:
```

```
      nextstate=S3;
```

```
    S3:
```

```
      nextstate=S4;
```

```
    S4:
```

```
      nextstate=S5;
```

```
    S5:
```

```
      nextstate=S6;
```

```
    S6:
```

```
      begin
```

```
        if(data!=8'h00)
```

```
          nextstate=S4;
```

```
        else
```

```
          nextstate=S7;
```


```
      end
```

```
    S7:
```

```
      nextstate=S0;
```

```
  endcase
```

```
end
```

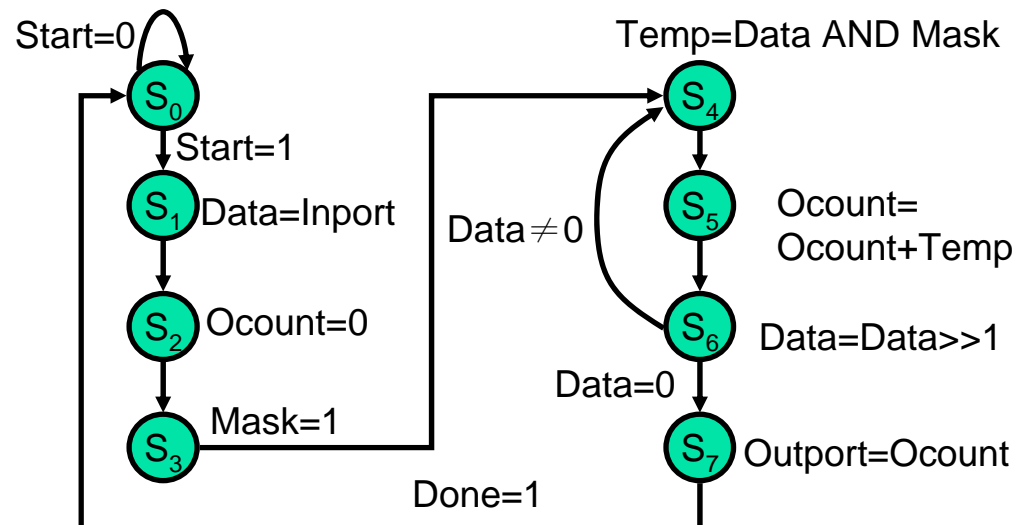

Controller of One's-Counter (8/8)

	IE	WR AD	READ AD A	READ AD B	ALU	SHIF T	O E
1	1	R ₁	X	X	X	X	0
2	0	R ₃	0	0	Add	Pass	0
3	0	R ₂	0	X	Inc	Pass	0
4	0	R ₄	R ₁	R ₂	AND	Pass	0
5	0	R ₃	R ₃	R ₄	Add	Pass	0
6	0	R ₁	R ₁	0	Add	Shift right	0
7	0	None	R ₃	0	Add	Pass	1

```
always@(currentstate)
```

```
begin
```

```
done=0;
```

Output Logic (Comb. C.)

```
case(currentstate)
```

```
S0:
```

```
control_word=20'b00XXX0XXX0XXXXXXXXXX0;
```

```
S1:
```

```
control_word=20'b110010XXX0XXXXXXXXXX0;
```

```
S2:
```

```
control_word=20'b010110XXX0XXX1010000;
```

```
S3:
```

```
control_word=20'b010100XXX1XXX1110000;
```

```
S4:
```

```
control_word=20'b01100100110100010000;
```

```
S5:
```

```
control_word=20'b01011101111001010000;
```

```
S6:
```

```
control_word=20'b0100110010XXX1011100;
```

```
S7:
```


```
begin
```

```
control_word=20'b00XXX10110XXX1010001;
```

```
done=1;
```


```
end endcase end endmodule
```

Traffic Light Controller (1/7)

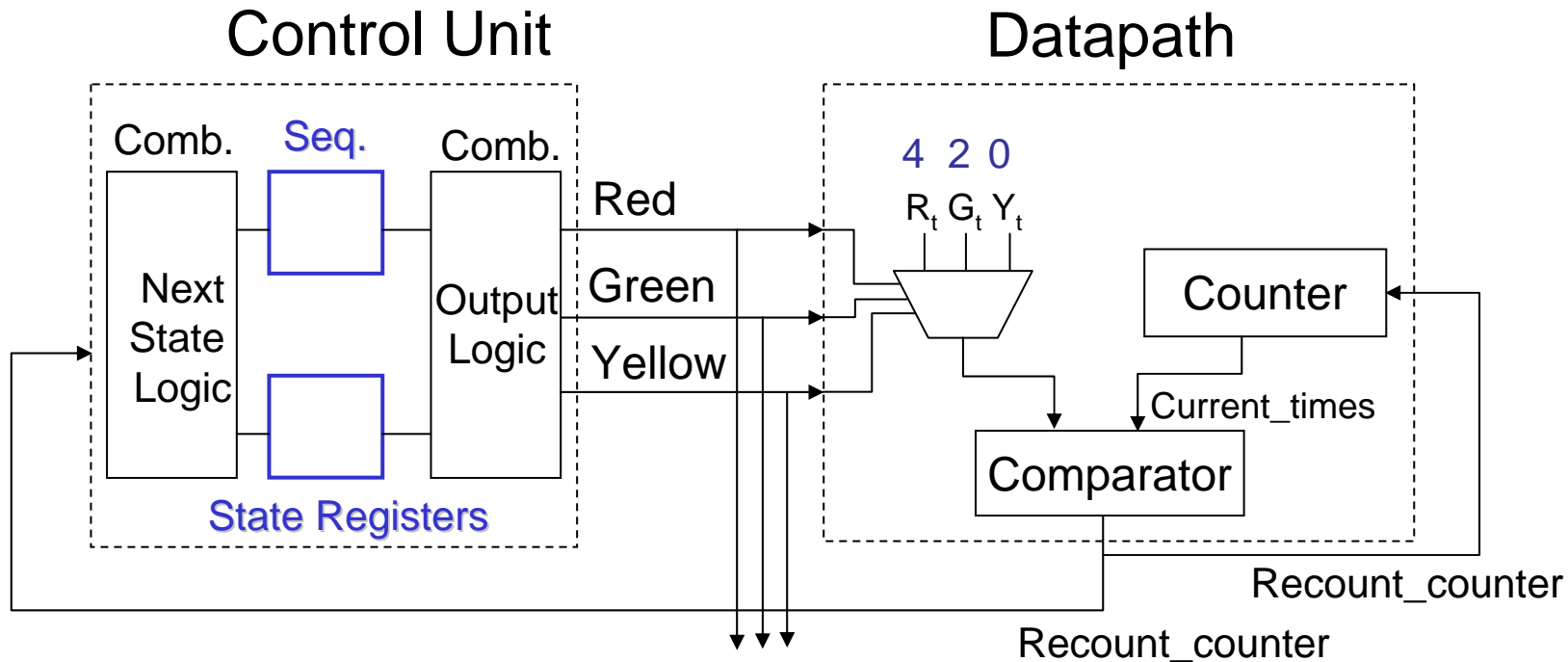

Input/Output

Recount_Counter16/Red Green Yellow

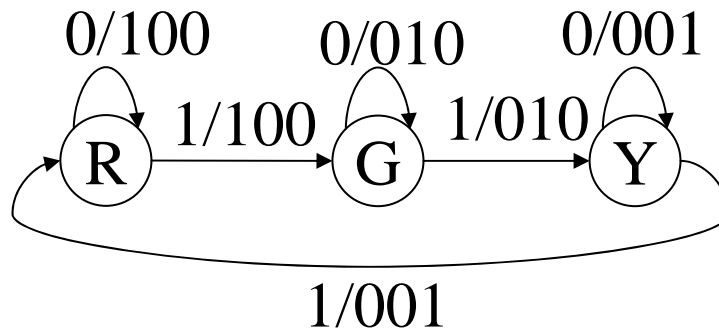

R_time: 4+1=5 cycles
 G_time: 2+1=3 cycles
 Y_time: 0+1=1 cycles



Traffic Light Controller (2/7)

```
module traffic(Clock,Reset,Red,Green,Yellow);  
input Clock,Reset; output Red,Green,Yellow;  
wire Recount_conter; wire [3:0] Counter_Number;
```

```
Traffic_Control (.Clock(Clock),.Reset(Reset),  
.Recount_Counter16(Recount_conter),.Red(Red),  
.Green(Green),.Yellow(Yellow));
```

```
Datapath (.Clock(Clock), .Reset(Reset), .RGY({Red,Green,Yellow}),  
.Recount(Recount_conter));
```

```
endmodule
```

```
module Datapath(Clock, Reset, RGY, Recount);  
input Clock, Reset; input [2:0] RGY;  
output Recount; wire [3:0] Counter_Number;
```

```
Compare A1(.current_times(Counter_Number), .RGY(RGY),  
.Recount_conter16(Recount));  
Counter16 A2(.Clock(Clock),.Reset(Reset),  
.Recount_Counter16(Recount),.Count_Out(Counter_Number));  
endmodule
```



Traffic Light Controller (3/7)

```
module Counter16(Clock,Reset,Recount_Counter16,
                Count_Out);
input Clock,Reset,Recount_Counter16;
output [3:0] Count_Out;
reg [3:0] Count_Out;

always@(posedge Clock)
begin
    if(Reset)
        Count_Out=0;
    else
        begin
            if(Recount_Counter16)
                Count_Out=0;
            else
                Count_Out=Count_Out+1;
        end
    end
end
endmodule
```



Traffic Light Controller (4/7)

```
module compare(current_times,
RGY, Recount_conter16);
input [2:0] RGY;
input [3:0] current_times;
output Recount_conter16;
reg Recount_conter16;
parameter R_times=4, G_times=2,
Y_times=0;

always @(RGY)
begin
    case(RGY)
        3'b100:begin
            if(current_times ==R_times)
                Recount_conter16=1;
            else
                Recount_conter16=0;
            end
    end
```

```
        3'b001:begin
            if(current_times ==Y_times)
                Recount_conter16=1;
            else
                Recount_conter16=0;
            end
        3'b010:begin
            if(current_times ==G_times)
                Recount_conter16=1;
            else
                Recount_conter16=0;
            end
        default: Recount_conter16=1;
    endcase
end
endmodule
```



Traffic Light Controller (5/7)

```
module Traffic_Control(Clock,Reset,
    Recount_Counter16,Red,Green,Yellow);
input Clock, Reset,Recount_Counter16;
output Red, Green, Yellow;
reg Red, Green, Yellow;
reg [1:0] currentstate,nextstate;

parameter [1:0] Red_Light=0, Green_Light=1,
    Yellow_Light=2;

always@(posedge Clock)
begin
    if(Reset)
        currentstate = Red_Light;
    else
        currentstate = nextstate;
end
```

State Register (Seq. C.)

```
always@(currentstate)
begin
    case(currentstate)
        Red_Light:begin
            if(Recount_Counter16)
                nextstate=Green_Light;
            else
                nextstate=Red_Light; end
        Green_Light:begin
            if(Recount_Counter16)
                nextstate=Yellow_Light;
            else
                nextstate=Green_Light; end
        Yellow_Light:begin
            if(Recount_Counter16)
                nextstate=Red_Light;
            else
                nextstate=Yellow_Light; end
        default: nextstate=Red_Light;
    endcase
end
```

Next State Logic (Comb. C.)



Traffic Light Controller (6/7)

```
always @(currentstate)
begin
  case(currentstate)
    Red_Light:begin
      Red=1'b1;
      Green=1'b0;
      Yellow=1'b0;
    end
    Green_Light:begin
      Red=1'b0;
      Green=1'b1;
      Yellow=1'b0;
    end
    Yellow_Light:begin
      Red=1'b0;
      Green=1'b0;
      Yellow=1'b1;
    end
  default:begin
    Red=1'b0;
    Green=1'b0;
    Yellow=1'b0;
  end
endcase
end
endmodule
```


Output Logic (Comb. C.)

Traffic Light Controller (7/7)

R_time: 4+1=5 cycles


G_time: 2+1=3 cycles

Y_time: 0+1=1 cycles

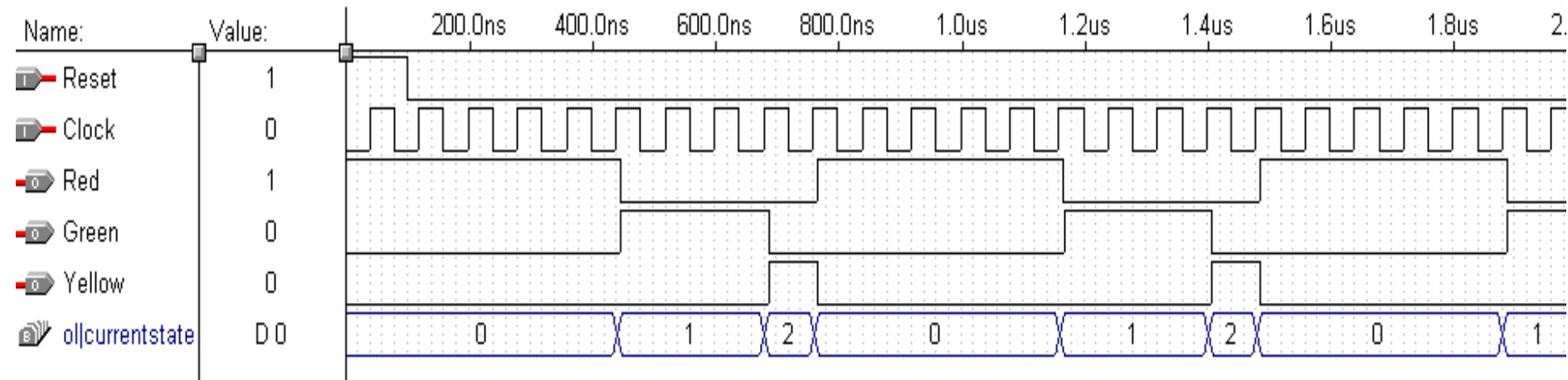


Input/Output Recount_Counter16/Red Green Yellow






 
Homework: Design traffic controller with Mealy machine



Video Tape Player (1/4)

 

Video Tape Player (2/4)

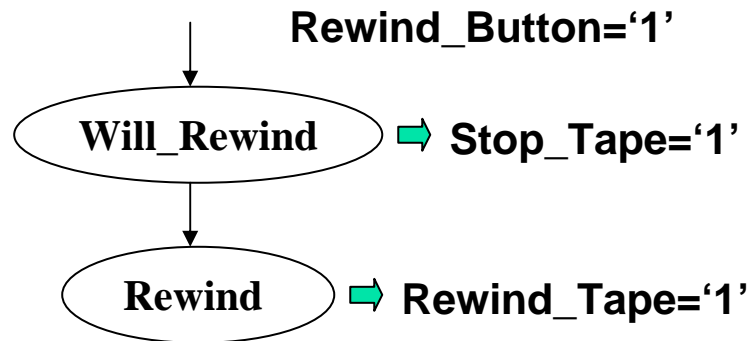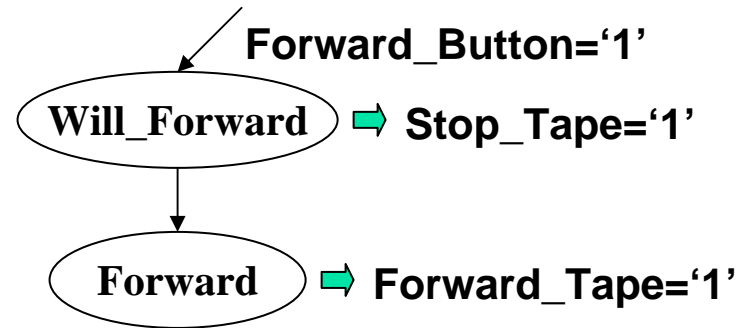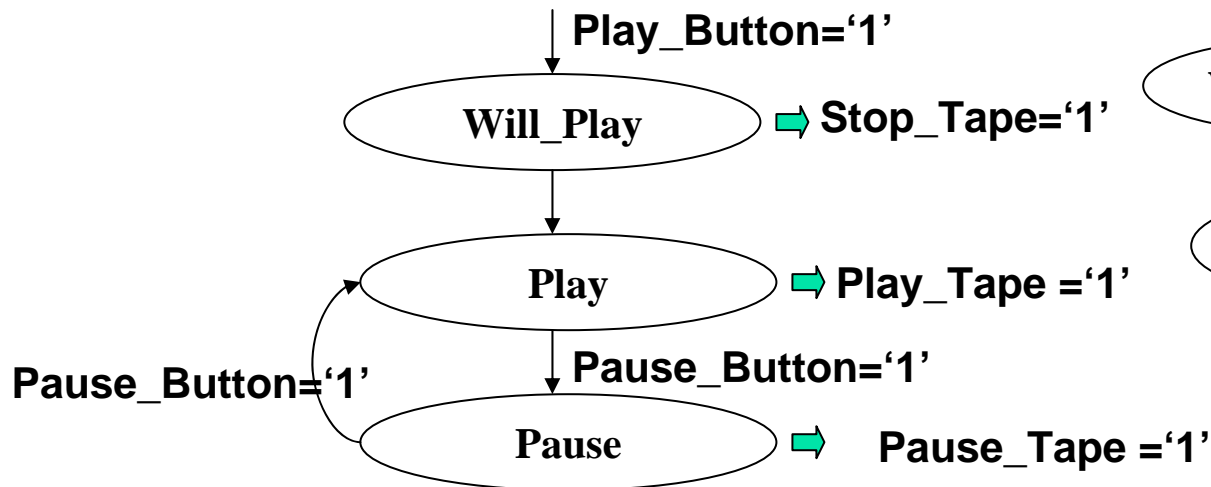   

Why needs will-XX state ?



Video Tape Player (3/4)

```
parameter STOP = 4'b0000, WILL_FORWARD = 4'b0001,  
FORWARD = 4'b0010, WILL_REWIND = 4'b0011,  
REWIND = 4'b0100, WILL_PLAY = 4'b0101,  
PLAY = 4'b0110, PAUSE = 4'b0111,  
WILL_RECORD = 4'b1000, RECORD = 4'b1001;
```

```
assign {Stop_Tape, Pause_Tape, Forward_Tape,  
Rewind_Tape, Play_Tape, Record_Tape} = outTape;
```

```
always @(posedge clk or posedge reset)
```

```
begin
```

```
    if(reset)
```

```
        curState = 0;
```

```
    else
```

```
        curState = nextState;
```

```
end
```

```
always @(curState)
```

```
begin
```

```
    case(curState)
```

```
        STOP: outTape = 6'b100000;
```

```
        WILL_FORWARD: outTape = 6'b100000;
```

```
        FORWARD: outTape = 6'b001000;
```

```
        WILL_REWIND: outTape = 6'b100000;
```

```
        REWIND: outTape = 6'b000100;
```

```
        WILL_PLAY: outTape = 6'b100000;
```

```
        PLAY: outTape = 6'b000010;
```

```
        PAUSE: outTape = 6'b010000;
```

```
        WILL_RECORD: outTape = 6'b100000;
```

```
        RECORD: outTape = 6'b000001;
```

```
        default: outTape = 6'b100000;
```

```
    endcase
```

```
end
```

Video Tape Player (4/4)

```
always @(curState or Stop_Button or
Pause_Button or Forward_Button or
Rewind_Button or Play_Button or Record_Button)
begin
    nextState = STOP;
    case(curState)
    STOP:
        nextState = STOP;
    WILL_FORWARD:
        nextState = FORWARD;
    FORWARD:
        nextState = FORWARD;
    WILL_REWIND:
        nextState = REWIND;
    REWIND:
        nextState = REWIND;
    WILL_PLAY:
        nextState = PLAY;
    PLAY:
        if(Pause_Button) nextState = PAUSE;
        else
            nextState = PLAY;
```

**will_forward, will_rewind,
will_play and will_record
are not affected by any
input buttons.
All input buttons are
pushed order-sensitive.**

```
    PAUSE: if(Pause_Button) nextState = PLAY;
           else nextState = PAUSE;
    WILL_RECORD:
        nextState = RECORD;
    RECORD:
        nextState = RECORD;
    endcase

    if(STOP || FORWARD || REWIND
    || PLAY || PAUSE || RECORD)
    begin
        if(Stop_Button)
            nextState = STOP;
        else if(Record_Button && Play_Button)
            nextState = WILL_RECORD;
        else if(Play_Button)
            nextState = WILL_PLAY;
        else if(Forward_Button)
            nextState = WILL_FORWARD;
        else if(Rewind_Button)
            nextState = WILL_REWIND;
    end
end
```